


Date :  
Time :  
Marks :

PHYSICS

## ALTERNATING CURRENT

### Single Correct Answer Type

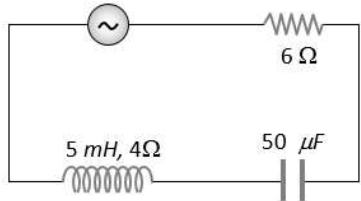1. In the circuit shown below, the ac source has voltage  $V = 20 \cos(\omega t)$  volts with  $\omega = 2000 \text{ rad/sec}$ . The amplitude of the current will be nearest to




- a) 2 A                      b) 3.3 A                      c)  $2/\sqrt{5} \text{ A}$                       d)  $\sqrt{5} \text{ A}$
2. For a series  $L - C - R$  circuit, the phase difference between current and voltage at the condition of resonance will be
- a)  $\frac{\pi}{2}$                       b)  $\frac{\pi}{4}$                       c) Zero                      d) Nothing can be said
3. An inductor is connected to an AC source. When compared to voltage, the current in the lead wires
- a) Is ahead in phase by  $\pi$                       b) Lags in phase by  $\pi$   
c) Is ahead in phase by  $\frac{\pi}{2}$                       d) Lags in phase by  $\frac{\pi}{2}$
4. Which of the following curves correctly represents the variation of capacitive reactance  $X_C$  with frequency  $f$
- a)

b)


c)

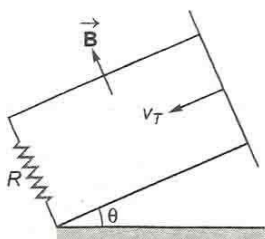d)
5. The impedance of a circuit consists of 3 ohm resistance and 4 ohm reactance. The power factor of the circuit is
- a) 0.4                      b) 0.6                      c) 0.8                      d) 1.0
6. In an AC series circuit, the instantaneous current is maximum when the instantaneous voltage is maximum. The circuit element connected to the source will be
- a) Pure inductor                      b) Pure capacitor  
c) Pure resistor                      d) Combination of capacitor and an inductor
7. What is self inductance of a coil which produces 5V, when current in it changes from 3 A to 2 A in one millisecond?
- a) 5000 H                      b) 5 mH                      c) 50 H                      d) 5 H
8.  $\frac{2.5}{\pi} \mu F$  capacitor and 3000-ohm resistance are joined in series to an ac source of 200 volt and  $50 \text{ sec}^{-1}$  frequency. The power factor of the circuit and the power dissipated in it will respectively be
- a) 0.6, 0.06 W                      b) 0.06, 0.6 W                      c) 0.6, 4.8 W                      d) 4.8, 0.6 W
9. A copper rod of mass  $m$  slides under gravity on two smooth parallel rails  $l$  distance apart and set at an angle  $\theta$  to the horizontal. At the bottom, the rails are joined by a resistance  $R$ , figure. There is a uniform magnetic field  $B$  perpendicular to the plane of the rails. The terminal velocity of the rod is




- a)  $\frac{mgR \tan \theta}{B^2 l^2}$       b)  $\frac{mgR \cot \theta}{B^2 l^2}$       c)  $\frac{mgR \sin \theta}{B^2 l^2}$       d)  $\frac{mgR \cos \theta}{B^2 l^2}$
10. An  $LCR$  circuit contains  $R = 50 \Omega$ ,  $L = 1 \text{ mH}$  and  $C = 0.1 \mu\text{F}$ . The impedance of the circuit will be minimum for a frequency of  
 a)  $\frac{10^5}{2\pi} \text{ s}^{-1}$       b)  $\frac{10^6}{2\pi} \text{ s}^{-1}$       c)  $2\pi \times 10^5 \text{ s}^{-1}$       d)  $2\pi \times 10^6 \text{ s}^{-1}$
11. An alternating  $\text{emf}$  is applied across a parallel combination of a resistance  $R$ , capacitance  $C$  and an inductance  $L$ . If  $I_R, I_L, I_C$  are the current through  $R, L$  and  $C$  respectively, then the diagram which correctly represents the phase relationship among  $I_R, I_L, I_C$  and source  $\text{emf } E$ , is given by  
 a)      b)      c)      d)
12. Power dissipated in an  $LCR$  series circuit connected to an a.c. source of  $\text{emf } E$  is  
 a)  $E^2 R / \left[ R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2 \right]$       b)  $\frac{E^2 \sqrt{R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2}}{R}$   
 c)  $\frac{E^2 \left[ R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2 \right]}{R}$       d)  $\frac{E^2 R}{\sqrt{R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2}}$
13. In the figure shown, three AC voltmeters are connected. At resonance,  
  
 a)  $V_2 = 0$       b)  $V_1 = 0$       c)  $V_3 = 0$       d)  $V_1 = V_2 \neq 0$
14. An electric bulb has a rated power of  $50 \text{ W}$  at  $100 \text{ V}$ . If it is used on an AC source  $200 \text{ V}$ ,  $50 \text{ Hz}$ , a choke has to be used in series with it. The should have an inductance of  
 a)  $0.1 \text{ mH}$       b)  $1 \text{ mH}$       c)  $0.1 \text{ H}$       d)  $1.1 \text{ H}$
15. An alternating current of frequency ' $f$ ' is flowing in a circuit containing a resistance  $R$  and a choke  $L$  in series. The impedance of this circuit is  
 a)  $R + 2\pi fL$       b)  $\sqrt{R^2 + 4\pi^2 f^2 L^2}$       c)  $\sqrt{R^2 + L^2}$       d)  $\sqrt{R^2 + 2\pi fL}$
16. A magnet is suspended lengthwise from a spring and while it oscillates, the magnet moves in and out of the coil  $C$  connected to a galvanometer  $G$ . Then as the magnet oscillates.  
 a)  $G$  shows no deflection      b)  $G$  shows deflection on one side  
 c) Deflection of  $G$  to the left and right has constant amplitude      d) Deflection of  $G$  to the left and right has decreasing amplitude
17. A transformer is having  $2100$  turns in primary and  $4200$  turns in secondary. An AC source of  $120 \text{ V}$ ,  $10 \text{ A}$  is connected to its primary. The secondary voltage and current are  
 a)  $240 \text{ V}, 5 \text{ A}$       b)  $120 \text{ V}, 10 \text{ A}$       c)  $240 \text{ V}, 10 \text{ A}$       d)  $120 \text{ V}, 20 \text{ A}$

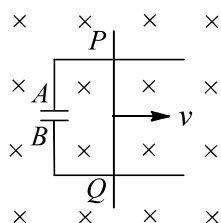
18. The current flowing in a step down transformer 220 V to 22 V having impedance  $220\ \Omega$  is  
 a) 1 A                                      b) 0.1 A                                      c) 2 mA                                      d) 0.1 mA
19. In order to obtain a time constant of 10 s in a  $R - C$  circuit containing a resistance of  $10^3\ \Omega$ , the capacity of the condenser should be  
 a)  $10\ \mu F$                                       b)  $100\ \mu F$                                       c)  $1000\ \mu F$                                       d)  $10000\ \mu F$
20. A conducting rod  $PQ$  of length  $L = 1.0\text{ m}$  is moving with a uniform speed  $v = 2.0\text{ ms}^{-1}$  in a uniform magnetic field  $= 4.0\text{ T}$  directed into the paper. A capacitor of capacity  $C = 10\ \mu F$  is connected as shown in figure. Then,



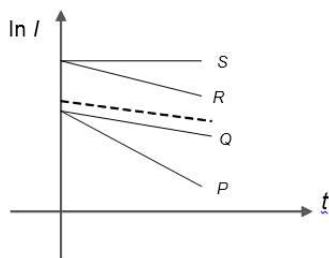- a)  $q_A = -80\ \mu C$  and  $q_B = +80\ \mu C$                                       b)  $q_A = +80\ \mu C$  and  $q_B = -80\ \mu C$   
 c)  $q_A = 0 = q_B$                                       d) Charge stored in the capacitor increases exponentially with time
21. In an  $L-C-R$  series AC circuit the voltage across  $L$ ,  $C$  and  $R$  is 10 V each. If the inductor is short circuited, the voltage across the capacitor would become  
 a) 10 V                                      b)  $\frac{20}{\sqrt{2}}\text{ V}$                                       c)  $20\sqrt{2}\text{ V}$                                       d)  $\frac{10}{\sqrt{2}}\text{ V}$
22. In an  $R-C$  circuit while charging, the graph of  $\ln I$  versus time is as shown by the dotted line in the adjoining diagram where  $I$  is the current. When the value of the resistance is doubled, which of the solid curves best represents the variation of  $\ln I$  versus time?



- a)  $P$                                       b)  $Q$                                       c)  $R$                                       d)  $S$
23. In the previous question, if the direction of  $i$  is reversed,  $(V_B - V_A)$  will be  
 a) 20 V                                      b) 15 V                                      c) 10 V                                      d) 5 V
24. A step-up transformer is used on a 120 V line to provide a potential difference of 2400 V. If the primary coil has 75 turns, the number of turns in the secondary coil is  
 a) 150                                      b) 1200                                      c) 1500                                      d) 1575
25. In a series  $L-C-R$  circuit  $R = 200\ \Omega$  and the voltage and the frequency of the main supply is 220V and 50 Hz respectively. On taking out the capacitance from the circuit the current lags behind the voltage by  $30^\circ$ . On taking out the inductor from the circuit the current leads the voltage by  $30^\circ$ . The power dissipated in the  $L-C-R$  circuit is  
 a) 305 W                                      b) 210 W                                      c) Zero                                      d) 242 W
26. In a  $LCR$  circuit having  $L = 8.0\text{ henry}$ ,  $C = 0.5\ \mu F$  and  $R = 100\text{ ohm}$  in series. The resonance frequency in per second is  
 a) 700 *radian*                                      b) 600 Hz                                      c) 500 *radian*                                      d) 500 Hz
27. An inductor of inductance  $L$  and resistor of resistance  $R$  are joined in series and connected by a source of frequency  $\omega$ . Power dissipated in the circuit is

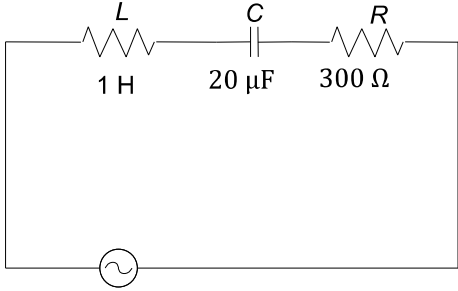
- a)  $\frac{(R^2 + \omega^2 L^2)}{V}$       b)  $\frac{V^2 R}{(R^2 + \omega^2 L^2)}$       c)  $\frac{V}{(R^2 + \omega^2 L^2)}$       d)  $\frac{\sqrt{R^2 + \omega^2 L^2}}{V^2}$
28. Which of the following quantities remains constant in a step-down transformer ?  
 a) Current      b) Voltage      c) Power      d) None of these
29. The root mean square value of the alternating current is equal to  
 a) Twice the peak value      b) Half the peak value  
 c)  $\frac{1}{\sqrt{2}}$  times the peak value      d) Equal to the peak value
30. The natural frequency of a  $L - C$  circuit is equal to  
 a)  $\frac{1}{2\pi} \sqrt{LC}$       b)  $\frac{1}{2\pi \sqrt{LC}}$       c)  $\frac{1}{2\pi} \sqrt{\frac{L}{C}}$       d)  $\frac{1}{2\pi} \sqrt{\frac{C}{L}}$
31. What is the self-inductance of a coil which produces 5 V when the current changes from 3 A to 2 A in one millisecond?  
 a) 5000 H      b) 5 mH      c) 50 H      d) 5 H
32. The power factor of good choke coil is  
 a) Nearly zero      b) Exactly zero      c) Nearly one      d) Exactly one
33. Two inductors of inductance  $L$  each are connected in series with opposite magnetic fluxes. What is the resultant inductance? (Ignore mutual inductance)  
 a) Zero      b)  $L$       c)  $2L$       d)  $3L$
34. A resistor of  $R = 6\Omega$ , an inductor of  $L = 1$  H and a capacitor of  $C = 17.36 \mu\text{F}$  are connected in series with an AC source. Find the  $Q$ -factor.  
 a) 3.72      b) 40      c) 2.37      d) 80
35. For a series  $L-C-R$  circuit at resonance, the statement which is not true is  
 a) Peak energy stored by a capacitor = peak energy stored by an inductor  
 b) Average power = apparent power  
 c) Wattless current is zero  
 d) Power factor is zero
36. An ac source of angular frequency  $\omega$  is fed across a resistor  $r$  and a capacitor  $C$  in series. The current registered is  $I$ . If the frequency of source is changed to  $\omega/3$  (maintaining the same voltage), the current in the circuit is found to be halved. Calculate the ratio of reactance to resistance at the original frequency  $\omega$   
 a)  $\sqrt{\frac{3}{5}}$       b)  $\sqrt{\frac{2}{5}}$       c)  $\sqrt{\frac{1}{5}}$       d)  $\sqrt{\frac{4}{5}}$
37. In Colpitt oscillator the feedback network consists of  
 a) Two inductors and a capacitor      b) Two capacitors and an inductor  
 c) Three pairs of  $R-C$  circuit      d) Three pairs of  $R-L$  circuit
38. In the  $L-C-R$  circuit shown, the impedance is
- 
- a) 500  $\Omega$       b) 300  $\Omega$       c) 100  $\Omega$       d) 200  $\Omega$
39. In an AC circuit the instantaneous values of emf and current are  
 $e = 200 \sin 300 t$  volt




and  $i = 2 \sin\left(300t + \frac{\pi}{3}\right)$  amp.

The average power consumed in watt is

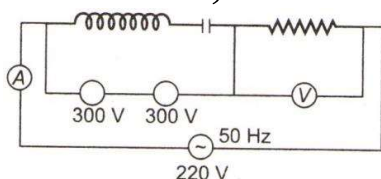
- a) 200                      b) 100                      c) 50                      d) 400
40. A current of 10 A in the primary coil of a circuit is reduced to zero. If the coefficient of mutual inductance is 3H and emf induced in secondary coil is 30 kV, time taken for the change of current is
- a)  $10^3$  s                      b)  $10^2$  s                      c)  $10^{-3}$  s                      d)  $10^{-2}$  s
41. A coil of inductance 300 mH and resistance  $2 \Omega$  is connected to a source of voltage 2V. The current reaches half of its steady state value in
- a) 0.05 s                      b) 0.1 s                      c) 0.15 s                      d) 0.3 s
42. The power factor of LCR circuit at resonance is
- a) 0.707                      b) 1                      c) Zero                      d) 0.5
43. In an ideal transformer, the voltage is stepped down from 11 kV to 220 V. If the primary current be 100 A, the current in the secondary should be
- a) 5 kA                      b) 1 kA                      c) 0.5 kA                      d) 0.1 kA
44. If a current  $I$  given by  $I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$  flows in an ac circuit across, which an ac potential of  $E = E_0 \sin \omega t$  has been applied, then the power consumption  $P$  in the circuit will be
- a)  $P = \frac{E_0 I_0}{\sqrt{2}}$                       b)  $P = \sqrt{2} E_0 I_0$                       c)  $P = \frac{E_0 I_0}{2}$                       d)  $P = 0$
45. In ac circuit of capacitance the current from potential is
- a) Forward                      b) Backward  
c) Both are in the same phase                      d) None of these
46. The frequency for which a  $5 \mu F$  capacitor has a reactance of  $\frac{1}{1000}$  ohm is given by
- a)  $\frac{100}{\pi}$  MHz                      b)  $\frac{1000}{\pi}$  Hz                      c)  $\frac{1}{1000}$  Hz                      d) 1000 Hz
47. An ac supply gives 30 V r. m. s. which passes through a  $10 \Omega$  resistance. The power dissipated in it is
- a)  $90\sqrt{2}$  W                      b) 90 W                      c)  $45\sqrt{2}$  W                      d) 45 W
48. The impedance of a R-C circuit is  $Z_1$  for frequency  $f$  and  $Z_2$  for frequency  $2f$ . Then,  $\frac{Z_1}{Z_2}$  is
- a) Between 1 and 2                      b) 2                      c) Between  $\frac{1}{2}$  and 1                      d)  $\frac{1}{2}$
49. If the capacity of a condenser is 1 F, then its resistance in a DC circuit will be
- a) Zero                      b) infinity                      c)  $1 \Omega$                       d)  $\frac{1}{2} \Omega$
50. In the circuit shown below what will be the readings of the voltmeter and ammeter? (Total impedance of circuit  $Z = 100 \Omega$ )



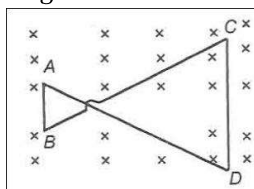
- a) 200 V, 1 A                      b) 800 V, 2 A                      c) 100 V, 2 A                      d) 220 V, 2.2 A
51. A conducting wire frame is placed in a magnetic field, which is directed into the paper, figure. The magnetic field is increasing at a constant rate. The directions of induced current in wires AB and CD are




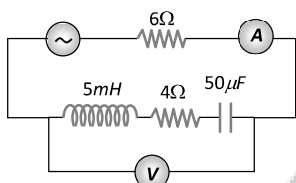- a)  $A$  to  $B$  and  $C$  to  $D$                       b)  $B$  to  $A$  and  $C$  to  $D$   
 c)  $A$  to  $B$  and  $D$  to  $C$                       d)  $B$  to  $A$  and  $D$  to  $C$
52. The quality factor of  $LCR$  circuit having resistance ( $R$ ) and inductance ( $L$ ) at resonance frequency ( $\omega$ ) is given by  
 a)  $\frac{\omega L}{R}$                       b)  $\frac{R}{\omega L}$                       c)  $\left(\frac{\omega L}{R}\right)^{1/2}$                       d)  $\left(\frac{\omega L}{R}\right)^2$
53. For a large industrial city with much load variations, the DC generator should be  
 a) Series wound                      b) Shunt wound                      c) Mixed wound                      d) Any
54. Choke coil works on the principle of  
 a) Transient current                      b) Self induction                      c) Mutual induction                      d) Wattless current
55. The potential difference  $V$  and the current  $i$  flowing through an instrument in an ac circuit of frequency  $f$  are given by  $V = 5 \cos \omega t$  volts and  $I = 2 \sin \omega t$  amperes (where  $\omega = 2\pi f$ ). The power dissipated in the instrument is  
 a) Zero                      b)  $10 \text{ W}$                       c)  $5 \text{ W}$                       d)  $2.5 \text{ W}$
56. A resistor  $R$ , an inductor  $L$  and a capacitor  $C$  are connected in series to an oscillator of frequency  $n$ , if the resonant frequency is  $n_r$ , then the current lags behind voltage, when  
 a)  $n = 0$                       b)  $n < n_r$                       c)  $n = n_r$                       d)  $n > n_r$
57. In  $AC$  series circuit, the resistance, inductive reactance and capacitive reactance are  $3\Omega$ ,  $10\Omega$  and  $14\Omega$  respectively. The impedance of the circuit is  
 a)  $5\Omega$                       b)  $4\Omega$                       c)  $7\Omega$                       d)  $10\Omega$
58. In the circuit shown in the figure, the ac source gives a voltage  $V = 20 \cos(2000t)$ . Neglecting source resistance, the voltmeter and ammeter reading will be




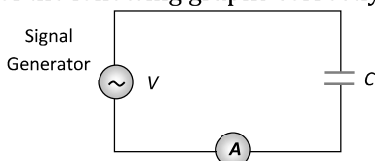- a)  $0\text{V}, 0.47\text{A}$                       b)  $1.68\text{V}, 0.47\text{A}$                       c)  $0\text{V}, 1.4\text{A}$                       d)  $5.6\text{V}, 1.4\text{A}$
59. A circuit draws  $330 \text{ W}$  from a  $110\text{V}$ ,  $60 \text{ Hz}$  AC line. The power factor is  $0.6$  and the current lags the voltage. The capacitance of a series capacitor that will result in a power factor of unity is equal to  
 a)  $31\mu\text{F}$                       b)  $54\mu\text{F}$                       c)  $151\mu\text{F}$                       d)  $201\mu\text{F}$
60. The primary winding of a transformer has  $200$  turns and its secondary winding has  $50$  turns. If the current in the secondary winding is  $40 \text{ A}$ , the current in the primary is  
 a)  $10 \text{ A}$                       b)  $80 \text{ A}$                       c)  $160 \text{ A}$                       d)  $800 \text{ A}$
61. An  $LC$  circuit contains a  $20 \text{ mH}$  inductor and a  $50 \mu\text{F}$  capacitor with an initial charge of  $10 \text{ mC}$ . The resistance of the circuit is negligible. Let the instant the circuit is closed be  $t = 0$ . At what time is the energy stored completely magnetic?  
 a)  $t = 0$                       b)  $t = 1.57 \text{ ms}$                       c)  $t = 3.14 \text{ ms}$                       d)  $t = 6.28 \text{ ms}$
62. An electric heater rated  $220 \text{ V}$  and  $550 \text{ W}$  is connected to A.C. mains. The current drawn by it is  
 a)  $0.8 \text{ A}$                       b)  $2.5 \text{ A}$                       c)  $0.4 \text{ A}$                       d)  $1.25 \text{ A}$
63. A constant voltage at different frequencies is applied across a capacitance  $C$  as shown in the figure. Which of the following graphs correctly depicts the variation of current with frequency



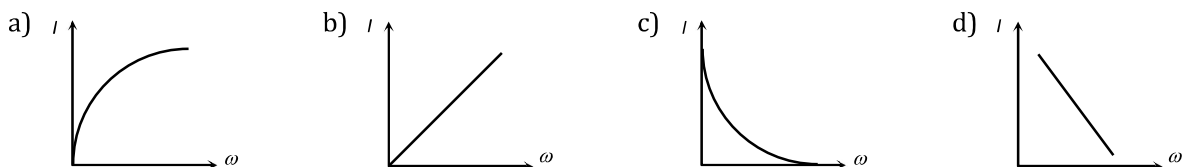


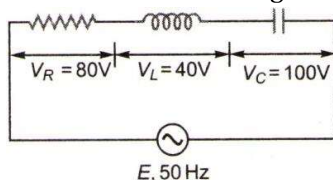64. The self inductance of the motor of an electric fan is  $10H$ . In order to impart maximum power at  $50\text{ Hz}$ , it should be connected to a capacitance of  
 a)  $1\ \mu F$                       b)  $2\ mF$                       c)  $4\ mF$                       d)  $8\ mF$
65. In an ideal choke, ratio of its inductance  $L$  to its DC resistance  $R$  is  
 a) Infinity                      b) Zero                      c) Unity                      d) hundred
66. The values of  $L$ ,  $C$  and  $R$  for a circuit are  $1H$ ,  $9F$  and  $3\Omega$ . What is the quality factor for the circuit at resonance?  
 a) 1                      b) 9                      c)  $\frac{1}{9}$                       d)  $\frac{1}{3}$
67. The value of alternating emf  $E$  in the given circuit will be




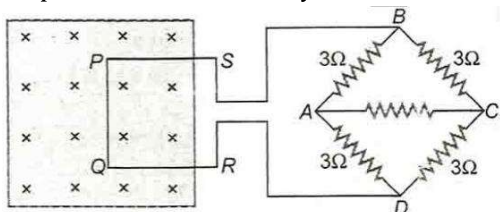- a) 220 V                      b) 140 V                      c) 100 V                      d) 20 V
68. An ac source is rated at  $220V, 50\text{ Hz}$ . The time taken for voltage to change from its peak value to zero is  
 a) 50 sec                      b) 0.02 sec                      c) 5 sec                      d)  $5 \times 10^{-3}\text{ sec}$
69. The expression for magnetic induction inside a solenoid of length  $L$ , carrying a current  $i$  and having  $N$  number of turns is  
 a)  $\frac{\mu_0 N}{4\pi L} i$                       b)  $\mu_0 N L i$                       c)  $\frac{\mu_0}{4\pi} N L i$                       d)  $\mu_0 \frac{N^2}{L} i$
70. If the total charge stored in the  $LC$  circuit is  $Q_0$ , then for  $t \geq 0$   
 a) The charge on the capacitor is  $Q = Q_0 \cos\left(\frac{\pi}{2} + \frac{t}{\sqrt{LC}}\right)$   
 b) The charge on the capacitor is  $Q = Q_0 \cos\left(\frac{\pi}{2} - \frac{t}{\sqrt{LC}}\right)$   
 c) The charge on the capacitor is  $Q = -LC \frac{d^2Q}{dt^2}$   
 d) The charge on the capacitor is  $Q = \frac{1}{\sqrt{LC}} \frac{d^2Q}{dt^2}$
71. A  $4\mu F$  capacitor, a resistance of  $2.5\ m\Omega$  is in series with  $12\text{ V}$  battery. Find the the time after which the potential difference across the capacitor is 3 times the potential difference across the resistor. [Given  $\ln(2)=0.693$ ]  
 a) 13.86 s                      b) 6.93 s                      c) 7 s                      d) 14 s
72. If  $E_0$  is the peak emf,  $I_0$  is the peak current and  $\phi$  is the phase difference between them, then the average power dissipation in the circuit is  
 a)  $\frac{1}{2} E_0 I_0$                       b)  $\frac{E_0 I_0}{\sqrt{2}}$                       c)  $\frac{1}{2} E_0 I_0 \sin \phi$                       d)  $\frac{1}{2} E_0 I_0 \cos \phi$
73. What is the self inductance of an air core solenoid  $1\text{ m}$  long, diameter  $0.05\text{m}$ , if it has 500 turns? Take  $\pi^2 = 10$ .  
 a)  $3.15 \times 10^{-4}\text{ H}$                       b)  $4.8 \times 10^{-4}\text{ H}$                       c)  $5 \times 10^{-4}\text{ H}$                       d)  $6.25 \times 10^{-4}\text{ H}$
74. If the coils of a transformer are made up of thick wire, then  
 a) Eddy currents loss will be more                      b) Magnetic flux leakage is reduced  
 c) Joule's heating loss is increased                      d) Joule's heating loss is reduced
75. A square metal wire loop  $PQRS$  of side  $10\text{ cm}$  and resistance  $1\ \Omega$  is moved with a constant velocity  $v_c$  in a uniform magnetic field of induction  $B = 2\text{ Wbm}^2$ , as shown in figure. The magnetic field lines are

perpendicular to the plane of the loop (directed into the paper). The loop is connected to network  $ABCD$  of resistors each of value  $3\ \Omega$ . The resistance of the lead wires  $SB$  and  $RD$  are negligible. The speed of the loop so as to have a steady current of  $\text{mA}$  in the loop is




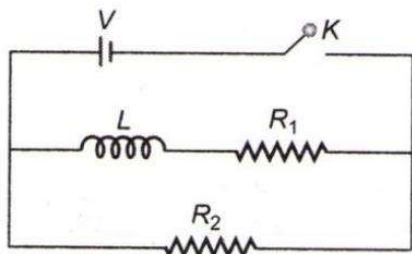- a)  $2\ \text{ms}^{-1}$       b)  $2 \times 10^{-2}\ \text{ms}^{-1}$       c)  $20\ \text{ms}^{-1}$       d)  $200\ \text{ms}^{-1}$
76. Let  $C$  be the capacitance of a capacitor discharging through a resistor  $R$ . Suppose  $t_1$  is the time taken for the energy stored in the capacitor to reduce to half its initial value and  $t_2$  is the time taken for the charge to reduce to one-fourth its initial value. Then the ratio  $\frac{t_1}{t_2}$  will be
- a) 1      b)  $\frac{1}{2}$       c)  $\frac{1}{4}$       d) 2
77. A series R-C circuit is connected to AC Voltage source. Consider two cases: (A) when  $C$  is without a dielectric medium and (B) when  $C$  is filled with dielectric of constant 4. The current  $I_R$  through the resistor and voltage  $V_C$  across the capacitor are compared in the two cases. Which of the following is/are true?
- a)  $I_R^A > I_R^B$       b)  $I_R^A < I_R^B$       c)  $V_C^A > V_C^B$       d)  $V_C^A < V_C^B$
78. Time constant of LC circuit is
- a)  $\frac{1}{2\pi LC}$       b)  $\frac{1}{2\pi L^2 C^2}$       c)  $\frac{LC}{2\pi}$       d)  $2\pi \sqrt{LC}$
79. Voltage  $V$  and current  $i$  in AC circuit are given by  
 $V = 50 \sin(50t)\text{volt}$   
 $i = 50 \sin\left(50t + \frac{\pi}{3}\right)\text{mA}$   
 The power dissipated in circuit is
- a) 5.0 W      b) 2.5 W      c) 1.25 W      d) zero
80. A resistance of 40 ohm and an inductance of 95.5 millihenry are connected in series in a 50 cycles/second ac circuit. The impedance of this combination is very nearly
- a) 30 ohm      b) 40 ohm      c) 50 ohm      d) 60 ohm
81. At high frequency, the capacitor offer
- a) More reactance      b) Less reactance      c) Zero reactance      d) Infinite reactance
82. In the circuit shown below, the key  $K$  is closed at  $t = 0$ . The current through the battery is



- a)  $\frac{VR_1R_2}{\sqrt{R_1^2 + R_2^2}}$  at  $t = 0$  and  $\frac{V}{R_2}$  at  $t = \infty$
- b)  $\frac{V}{R_2}$  at  $t = 0$  and  $\frac{V(R_1+R_2)}{R_1R_2}$  at  $t = \infty$
- c)  $\frac{V}{R_2}$  at  $t = 0$  and  $\frac{VR_1R_2}{\sqrt{R_1^2 + R_2^2}}$  at  $t = \infty$
- d)  $\frac{V(R_1+R_2)}{R_1R_2}$  at  $t = 0$  and  $\frac{V}{R_2}$  at  $t = \infty$

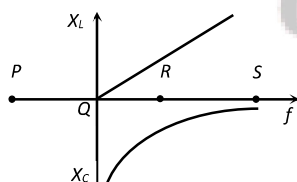
83. A resistor and a capacitor are connected in series with an AC source. If the potential drop across the capacitor is 5 V and that across resistor is 12 V, then applied voltage is  
a) 13 V                      b) 17 V                      c) 5 V                      d) 12 V
84. In an A.C. circuit the current  
a) Always leads the voltage                      b) Always lags behind the voltage  
c) Is always in phase with the voltage                      d) May lead or lag behind or be in phase with the voltage
85. An LCR series circuit with  $R = 100\Omega$  is connected to a 200 V, 50 Hz a.c. source when only the capacitance is removed, the current leads the voltage by  $60^\circ$ . When only the inductance is removed, the current leads the voltage by  $60^\circ$ . The current in the circuit is  
a) 2A                      b) 1A                      c)  $\frac{\sqrt{3}}{2}A$                       d)  $\frac{2}{\sqrt{3}}A$
86. The ratio of turns in primary and secondary coils of a transformer is 1 : 20. The ratio of currents in primary and secondary coils will be  
a) 1 : 20                      b) 20 : 1                      c) 1 : 400                      d) 400 : 1
87. If number of turns in primary and secondary coils is increased to two times each, the mutual inductance  
a) Becomes 4 times                      b) Becomes 2 times  
c) Becomes 1 /4 times                      d) Remains unchanged
88. A generator produces a voltage that is given by  $V = 240 \sin 120 t$ , where  $t$  is in seconds. The frequency and r. m. s. voltage are  
a) 60 Hz and 240 V                      b) 19 Hz and 120 V                      c) 19 Hz and 170 V                      d) 754 Hz and 70 V
89. A 0.7 henry inductor is connected across a 120V – 60 Hz ac source. The current in the inductor will be very nearly  
a) 4.55 amp                      b) 0.355 amp                      c) 0.455 amp                      d) 3.55 amp
90. The peak value of 220 volts of ac mains is  
a) 155.6 volts                      b) 220.0 volts                      c) 311.0 volts                      d) 440 volts
91. The resonance point in  $X_L - f$  and  $X_C - f$  curves is




- a) P                      b) Q                      c) R                      d) S
92. The impedance of a circuit, when a resistance  $R$  and an inductor of inductance  $L$  are connected in series in an AC circuit of frequency  $f$ , is  
a)  $\sqrt{R + 2\pi^2 f^2 L^2}$                       b)  $\sqrt{R + 4\pi^2 f^2 L^2}$                       c)  $\sqrt{R^2 + 4\pi^2 f^2 L^2}$                       d)  $\sqrt{R^2 + 2\pi^2 f^2 L^2}$
93. Two coils are at fixed locations. When coil 1 has no current and the current in the coil 2 increases at the rate  $15.0 \text{ As}^{-1}$ , the emf in coil 1 is 25.0 mV. When coil 2 has no current of 3.6 A. The flux linkage in coil 2  
a) 4 mWb                      b) 6 mWb                      c) 10 mWb                      d) 16 mWb
94. In a L-C-R series circuit, the potential difference between the terminals of the inductance is 60 V, between the terminals of the capacitor is 30 V and that across the resistance is 40 V. Then, supply voltage will be equal to  
a) 50 V                      b) 70 V                      c) 130 V                      d) 10 V
95. The voltage of an ac supply varies with time ( $t$ ) as  $V = 120 \sin 100\pi t \cos 100\pi t$ . The maximum voltage and frequency respectively are  
a) 12 volts, 100 Hz                      b)  $\frac{120}{\sqrt{2}}$  volts, 100 Hz                      c) 60 volts, 200 Hz                      d) 60 volts, 100 Hz
96. The self inductance of a choke coils is 10 mH. When it is connected with a 10V dc source, then the loss of

power is 20 watt. When it is connected with 10 volt ac source loss of power is 10 watt. The frequency of ac source will be

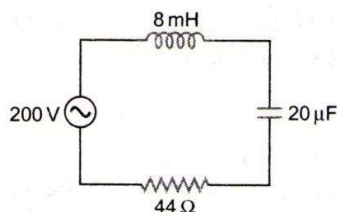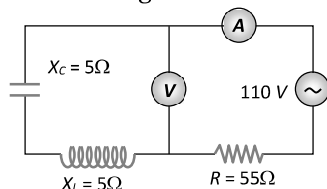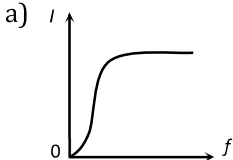
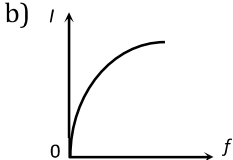

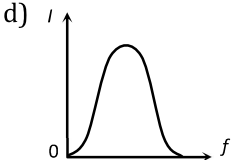
- a) 50 Hz                      b) 60 Hz                      c) 80 Hz                      d) 100 Hz
97. An ideal choke draws a current of 8 A when connected to an AC supply of 100 V, 50 Hz. A pure resistor draws a current of 10 A when connected to the same source. The ideal choke and the resistor are connected in series and then connected to the AC source of 150 V, 40 Hz. The current in the circuit becomes
- a)  $\frac{15}{\sqrt{2}}$  A                      b) 8 A                      c) 18 A                      d) 10 A
98. In an  $L - C - R$  circuit, capacitance is changed from  $C$  to  $2C$ . For the resonant frequency to remain unchanged, the inductance should be changed from  $L$  to
- a)  $4L$                       b)  $2L$                       c)  $L/2$                       d)  $L/4$
99. The instantaneous value of current in an A.C. circuit is  $I = 2 \sin(100 \pi t + \pi/3)$  A. The current will be maximum for the first time at
- a)  $t = \frac{1}{100}$  s                      b)  $t = \frac{1}{200}$  s                      c)  $t = \frac{1}{400}$  s                      d)  $t = \frac{1}{600}$  s
100. For the series  $L - C - R$  circuit shown in the figure, what is the resonance frequency and the amplitude of the current at the resonating frequency?




- a)  $2500 \text{ rads}^{-1}$  and  $5\sqrt{2}$  A                      b)  $2500 \text{ rads}^{-1}$  and 5 A
- c)  $2500 \text{ rads}^{-1}$  and  $\frac{5}{\sqrt{2}}$  A                      d)  $250 \text{ rads}^{-1}$  and  $5\sqrt{2}$  A
101. A bulb is connected first with dc and then ac of same voltage it will shine brightly with
- a) AC                      b) DC
- c) Brightness will be in ratio 1/1.4                      d) Equally with both
102. In an ac circuit, the r. m. s. value of current,  $I_{rms}$  is related to the peak current,  $I_0$  by the relation
- a)  $I_{rms} = \frac{1}{\pi} I_0$                       b)  $I_{rms} = \frac{1}{\sqrt{2}} I_0$                       c)  $I_{rms} = \sqrt{2} I_0$                       d)  $I_{rms} = \pi I_0$
103. The reading of ammeter in the circuit shown will be



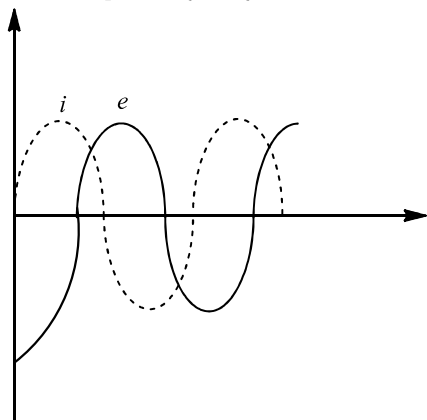- a) 2 A                      b) 2.4 A                      c) Zero                      d) 1.7 A
104. A fully charged capacitor  $C$  with initial charge  $q_0$  is connected to a coil of self inductance  $L$  at  $t = 0$ . The time at which the energy is stored equally between the electric and the magnetic fields is
- a)  $\frac{\pi}{4} \sqrt{LC}$                       b)  $2\pi \sqrt{LC}$                       c)  $\sqrt{LC}$                       d)  $\pi \sqrt{LC}$
105. The phase difference between the current and voltage of  $LCR$  circuit in series combination at resonance is
- a) 0                      b)  $\pi/2$                       c)  $\pi$                       d)  $-\pi$
106. In an  $L - C - R$  series AC circuit, the voltage across each of the components.  $L$ ,  $C$  and  $R$  is 50 V. The voltage across the  $L - C$  combination will be
- a) 50 V                      b)  $50\sqrt{2}$  V                      c) 100 V                      d) zero
107. In an induction coil, the coefficient of mutual inductance is 4H. If current of 5A in the primary coil is cut off


- $i = 1/1500$  s, the emf at the terminals of the secondary coil will be  
 a) 15 kV                      b) 60 kV                      c) 10 kV                      d) 30 kV
108. The maximum value of AC voltage in a circuit is 707 V. Its rms value is  
 a) 70.7 V                      b) 100 V                      c) 500 V                      d) 707 V
109. A metal rod of resistance  $20\ \Omega$  is fixed along a diameter of a conducting ring of radius 0.1 m and lies on  $x - y$  plane. There is a magnetic field  $\vec{B} = (50\ \text{T}) \hat{k}$ . The ring rotates with an angular velocity  $\omega = 20\ \text{rads}^{-1}$  about its axis. An external resistance of  $10\ \Omega$  is connected across the centre of the ring and rim. The current through external resistance is  
 a)  $\frac{1}{2}$  A                      b)  $\frac{1}{3}$  A                      c)  $\frac{1}{4}$  A                      d) zero
110. An ac source of variable frequency  $f$  is connected to an  $LCR$  series circuit. Which of the graphs in figure represents the variation of current  $I$  in the circuit with frequency  $f$   
 a)       b)       c)       d) 
111. A coil of resistance  $R$  and inductance  $L$  is connected to a battery of emf  $E$  volt. The final current in the coil is  
 a)  $\frac{E}{R}$                       b)  $\frac{E}{L}$                       c)  $\sqrt{\left(\frac{E}{R^2 + L^2}\right)}$                       d)  $\sqrt{\left(\frac{EL}{R^2 + L^2}\right)}$
112. An alternating e.m.f. is applied to purely capacitive circuit. The phase relation between e.m.f. and current flowing in the circuit is **or**  
 In a circuit containing capacitance only  
 a) e.m.f. is ahead of current by  $\pi/2$                       b) Current is ahead of e.m.f. by  $\pi/2$   
 c) Current lags behind e.m.f. by  $\pi$                       d) Current is ahead of e.m.f. by  $\pi$
113. What is the value of inductance  $L$  for which the current is a maximum in a series  $L-C-R$  circuit with  $C = 10\ \mu\text{F}$  and  $\omega = 1000\ \text{s}^{-1}$ ?  
 a) 100 mH                      b) 1 mH  
 c) Cannot be calculated unless  $R$  is known                      d) 10 mH
114. What will be the self inductance of a coil, to be connected in a series with a resistance of  $\pi\sqrt{3}\ \Omega$  such that the phase difference between the emf and the current at 50 Hz frequency is  $30^\circ$   
 a) 0.5 henry                      b) 0.03 henry                      c) 0.05 henry                      d) 0.01 henry
115. When an AC source of emf  $e = E_0 \sin(100t)$  is connected across a circuit, the phase difference between the emf  $e$  and the current  $i$  in the circuit is observed to be  $\frac{\pi}{4}$ , as shown in the diagram. If the circuit consists possibly only of  $R - C$  or  $R - L$  or  $L - C$  in series, find the relationship between the two elements



- a)  $R = 1\ \text{k}\Omega, C = 10\ \mu\text{F}$       b)  $R = 1\ \text{k}\Omega, C = 1\ \mu\text{F}$       c)  $R = 1\ \text{k}\Omega, L = 10\ \text{H}$       d)  $R = 1\ \text{k}\Omega, L = 1\ \text{H}$




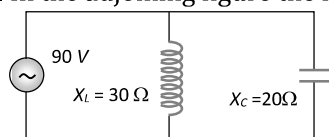116. The current in series  $LCR$  circuit will be maximum when  $\omega$  is  
 a) As large as possible  
 b) Equal to natural frequency of  $LCR$  system  
 c)  $\sqrt{LC}$   
 d)  $\sqrt{1/LC}$
117. Three identical ring move with the same speed on a horizontal surface in a uniform horizontal magnetic field normal to the planes of the rings. The first (A) slips without rolling, the second (B) rolls without slipping, and the third rolls with slipping  
 a) The same emf is induced in all the three rings  
 b) No emf is induced in any of the rings  
 c) In each ring, all points are at the same potential  
 d) B develops the maximum induced emf, and A the least.
118. An alternating voltage  $e = 200 \sin 100 t$  is applied to a series combination  $R = 30 \Omega$  and an inductor of 400 mH. The power factor of the circuit is  
 a) 0.01  
 b) 0.2  
 c) 0.05  
 d) 0.6
119. An alternating e.m.f. of angular frequency  $\omega$  is applied across an inductance. The instantaneous power developed in the circuit has an angular frequency  
 a)  $\omega/4$   
 b)  $\omega/2$   
 c)  $\omega$   
 d)  $2\omega$
120. The peak value of an alternating emf  $E$  given by  $E = E_0 \cos \omega t$  is 10 V and its frequency is 50 Hz. At a time  $t = \frac{1}{100}$  s, the instantaneous value of the emf is  
 a) 10 V  
 b)  $5\sqrt{3}$  V  
 c) 5 V  
 d) 1 V
121. An alternating voltage (in volt) given by  $V = 200\sqrt{2} \sin(100t)$  is connected to  $1\mu F$  capacitor through an AC ammeter. The reading of the ammeter will be  
 a) 10 mA  
 b) 20 mA  
 c) 40 mA  
 d) 80 mA
122. In an AC circuit,  $V$  and  $I$  are given by  $V = 150 \sin(150t)$  volt and  $I = 150 \sin\left(150t + \frac{\pi}{3}\right)$  amp. The power dissipated in the circuit is  
 a) Zero  
 b) 5625 W  
 c) 150 W  
 d) 106 W
123. The resonance frequency of the tank circuit of an oscillator when  $L = \frac{10}{\pi^2}$  mH and  $C = 0.04 \mu F$  are connected in parallel is  
 a) 250 kHz  
 b) 25 kHz  
 c) 2.5 kHz  
 d) 25 MHz
124. The process by which ac is converted into dc is known as  
 a) Purification  
 b) Amplification  
 c) Rectification  
 d) Current amplification
125. In the adjoining figure the impedance of the circuit will be



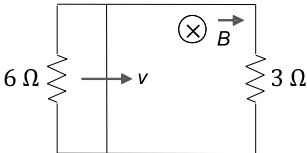- a) 120 ohm  
 b) 50 ohm  
 c) 60 ohm  
 d) 90 ohm
126. An emf is 15 V is applied in a circuit coil containing 5 H inductance and  $10 \Omega$  resistance. The ratio of currents at time  $t = \infty$  and  $t = 1$  s is  
 a)  $\frac{e^{1/2}}{e^{1/2} - 1}$   
 b)  $\frac{e^2}{e^2 - 1}$   
 c)  $1 - e^{-1}$   
 d)  $e^{-1}$
127. A transformer is used to light 140 W, 24 V lamp from 240 V AC mains. The current in the mains is 0.7 A. The efficiency of transformer is nearest to  
 a) 90%  
 b) 80%  
 c) 70%  
 d) 60%
128. Eddy current are produced when  
 a) A metal is kept in varying magnetic field  
 b) A metal is kept in steady magnetic field  
 c) A circular coil is placed in a magnetic field  
 d) Through a circular coil, current is passed
129. An inductive circuit contains a resistance of 10 ohm and an inductance of 2.0 henry. If an ac voltage of 120 volt and frequency of 60 Hz is applied to this circuit, the current in the circuit would be nearly  
 a) 0.32 amp  
 b) 0.16 amp  
 c) 0.48 amp  
 d) 0.80 amp




130. The instantaneous values of current and voltage in an ac circuit are  $i = 100 \sin 314 t$  amp and  $e = 200 \sin (314 t + \pi/3)$  V respectively. If the resistance is  $1 \Omega$ , then the reactance of the circuit will be  
 a)  $-200\sqrt{3} \Omega$                       b)  $\sqrt{3} \Omega$                       c)  $-200\sqrt{3} \Omega$                       d)  $100\sqrt{3} \Omega$
131. Alternating current cannot be measured by DC ammeter because  
 a) AC cannot pass through DC ammeter  
 b) AC changes direction  
 c) Average value of current for complete cycle is zero  
 d) DC ammeter will get damaged
132. A voltage of peak value 283 V and varying frequency is applied to a series  $L - C - R$  combination in which  $R = 3 \Omega$ ,  $L = 25$  mH and  $C = 400 \mu\text{F}$ . The frequency (in Hz) of the source at which maximum power is dissipated in the above, is  
 a) 51.5                      b) 50.7                      c) 51.1                      d) 50.3
133. A choke coil has  
 a) High inductance and low resistance                      b) Low inductance and high resistance  
 c) High inductance and high resistance                      d) Low inductance and low resistance
134. The number of turns in the primary coil of a transformer is 200 and the number of turns in secondary coil is 10. If 240 V AC is applied to the primary, the output from secondary will be  
 a) 48 V                      b) 24 V                      c) 12 V                      d) 6 V
135. If an  $8 \Omega$  resistance and  $6 \Omega$  reactance are present in an ac series circuit then the impedance of the circuit will be  
 a)  $20 \text{ ohm}$                       b)  $5 \text{ ohm}$                       c)  $10 \text{ ohm}$                       d)  $14\sqrt{2} \text{ ohm}$
136. In an ac circuit with voltage  $V$  and current  $I$ , the power dissipated is  
 a)  $VI$                       b)  $\frac{1}{2}VI$   
 c)  $\frac{1}{\sqrt{2}}VI$                       d) Depends on the phases between  $V$  and  $I$
137. In an AC circuit, the instantaneous values of emf and current are  $e = 200 \sin 314t$  volt and  $i = \sin (314t + \frac{\pi}{3})$  amp. The average power consumed in watt is  
 a) 200                      b) 100                      c) 50                      d) 25
138. In a region of uniform magnetic induction  $B = 10^{-2}$  tesla, a circular coil of radius 30 cm and resistance  $\pi^2 \text{ ohm}$  is rotated about an axis which is perpendicular to the direction of  $B$  and which forms a diameter of the coil. If the rotates at 200 rpm the amplitude of the alternating current induced in the coil is  
 a)  $4\pi^2 \text{ mA}$                       b)  $30 \text{ mA}$                       c)  $6 \text{ mA}$                       d)  $200 \text{ mA}$
139. A rectangular loop with a sliding connector of length  $l = 1.0$  m is situated in a uniform magnetic field  $B = 2\text{T}$ . Perpendicular to the plane of loop. Resistance of connector is  $r = 2\Omega$ . Two resistance of  $6 \Omega$  and  $3 \Omega$  are connected as shown in figure. The external force required to keep the connector moving with a constant velocity  $v = 2 \text{ ms}^{-1}$  is
- 
- a) 2 N                      b) 1 N                      c) 4 N                      d) 6 N
140. An AC voltage source has an output of  $\Delta V = (200\text{V}) \sin 2\pi ft$ . This source is connected to a  $100 \Omega$  resistor. RMS current in the resistance is  
 a) 1.41 A                      b) 2.41 A                      c) 3.41 A                      d) 0.71 A
141. The average power dissipated in a pure inductor of inductance  $L$  when an ac current is passing through it, is  
 (Inductance of the coil  $L$  and current  $I$ )

- a)  $\frac{1}{2}LI^2$                       b)  $\frac{1}{4}LI^2$                       c)  $2Li^2$                       d) Zero

142. The time taken by AC of 50 Hz in reaching from zero to the maximum value is

- a)  $50 \times 10^{-3}$  s                      b)  $5 \times 10^{-3}$  s                      c)  $1 \times 10^{-3}$  s                      d)  $2 \times 10^{-3}$  s

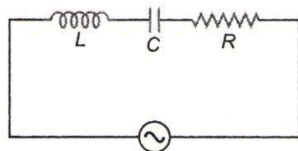143. A 100 V, AC source of frequency 500 Hz is connected to an  $L$ - $C$ - $R$  circuit with  $L=8.1$  mH,  $C = 12.5$   $\mu$ F,  $R = 10$   $\Omega$  all connected in series as shown in figure. What is the quality factor of circuit?



- a) 2.02                      b) 2.5434                      c) 20.54                      d) 200.54

144. Two coils  $A$  and  $B$  have coefficient of mutual inductance  $M = 2$  H. The magnetic flux passing through coil  $A$  changes by 4 Wb in 10 s due to change in current in  $B$ . Then

- a) Change in current in  $B$  in this time interval is 0.5 A    b) Change in current in  $B$  in this time interval is 8 A  
c) The change in current in  $B$  in this time interval is 2 d) A change in current of 1 A in coil  $A$  will produce a change in flux passing through  $B$  by 4 Wb


145. In an  $LCR$  circuit  $R = 100$  ohm. When capacitance  $C$  is removed, the current lags behind the voltage by  $\pi/3$ . When inductance  $L$  is removed, the current leads the voltage by  $\pi/3$ . The impedance of the circuit is

- a) 50 ohm                      b) 100 ohm                      c) 200 ohm                      d) 400 ohm

146. The instantaneous values of current and emf in an ac circuit are  $I = 1/\sqrt{2} \sin 314 t$  amp and  $E = \sqrt{2} \sin(314 t - \pi/6)$  V respectively. The phase difference between  $E$  and  $I$  will be

- a)  $-\pi/6$  rad                      b)  $-\pi/3$  rad                      c)  $\pi/6$  rad                      d)  $\pi/3$  rad

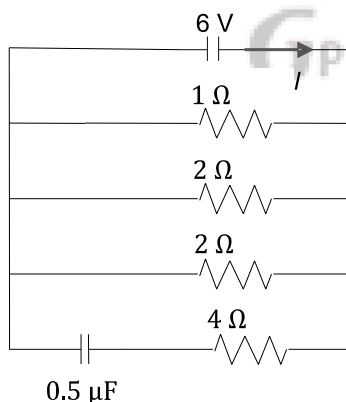147. In the given circuit diagram the current through the battery and the charge on the capacitor respectively in steady state are




- a) 1 A and 3  $\mu$ C                      b) 17 A and 0  $\mu$ C                      c)  $\frac{6}{7}$  A and  $\frac{12}{7}$   $\mu$ C                      d) 11 A and 3  $\mu$ C

148. In a  $L - R$  circuit, the value of  $L$  is  $\left(\frac{0.4}{\pi}\right)$  H and the value of  $R$  is 30  $\Omega$ . If in the circuit, an alternating emf of 200 V at 50 cycle/s is connected, the impedance of the circuit and current will be

- a) 11.4  $\Omega$ , 17.5 A                      b) 30.7  $\Omega$ , 6.5 A                      c) 40.4  $\Omega$ , 5 A                      d) 50  $\Omega$ , 4 A

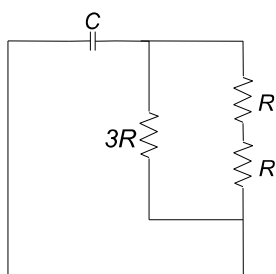149. The time constant of the given circuit is



- a)  $\frac{3RC}{5}$       b)  $\frac{6RC}{5}$       c)  $\frac{5RC}{6}$       d) None of these

150. A bulb and a capacitor are in series with an ac source. On increasing frequency how will glow of the bulb change

- a) The glow decreases      b) The glow increases  
c) The glow remain the same      d) The bulb quenches

151. An  $L - C - R$  circuit of  $R = 100 \Omega$  is connected to an AC source 100 V, 50 Hz. The magnitude of phase difference between current and voltage is  $30^\circ$ . The power dissipated in the  $L - C - R$  circuit is

- a) 50 W      b) 86.6 W      c) 100 W      d) 200 W

152. The time taken by an alternating current of 50 Hz in reaching from zero to its maximum value will be

- a) 0.5 s      b) 0.005 s      c) 0.05 s      d) 5 s

153. The voltage of domestic ac is 220 volt. What does the represent

- a) Mean voltage      b) Peak voltage  
c) Root mean voltage      d) Root mean square voltage

154. If the value of potential in an ac circuit is 10V, then the peak value of potential is

- a)  $\frac{10}{\sqrt{2}}$       b)  $10\sqrt{2}$       c)  $20\sqrt{2}$       d)  $\frac{20}{\sqrt{2}}$

155. Which of the following components of a  $L - C - R$  circuit, with AC supply, dissipates energy?

- a)  $L$       b)  $R$       c)  $C$       d) All of these

156. In an AC circuit the emf( $e$ ) and the current ( $i$ ) at any instant are given respectively by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of AC is

- a)  $\frac{E_0 I_0}{2}$       b)  $\frac{E_0 I_0}{2} \sin \phi$       c)  $\frac{E_0 I_0}{2} \cos \phi$       d)  $E_0 I_0$

157. In a current carrying long solenoid, the field produced does not depend upon

- a) Number of turns per unit length      b) Current flowing  
c) Radius of solenoid      d) All of the above

158. In a series combination  $R = 300 \Omega$ ,  $L = 0.9H$ ,  $C = 2.0 \mu F$ ,  $\omega = 1000 \text{ rads}^{-1}$ , the impedance of the circuit is

- a)  $1300 \Omega$       b)  $900 \Omega$       c)  $500 \Omega$       d)  $400 \Omega$

159. Average power in the  $L-C-R$  circuit depends upon

- a) Current      b) phase difference only  
c) Emf      d) Current, emf and phase difference

160. In  $L - C - R$  circuit, an alternating emf of angular frequency  $\omega$  is applied then the total impedance will be

- a)  $\left[ (R\omega)^2 + \left( L\omega - \frac{1}{C\omega} \right)^2 \right]^{1/2}$       b)  $\left[ R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2 \right]^{-1/2}$   
c)  $[R^2 + (L\omega - C\omega)^2]^{1/2}$       d)  $\left[ R^2 + \left( L\omega - \frac{1}{C\omega} \right)^2 \right]^{1/2}$


161. A capacitor  $50 \mu F$  is connected to a supply of 220 V and angular frequency  $50 \text{ rad s}^{-1}$ . The value of rms current in the circuit is

- a) 0.45 A      b) 0.50 A      c) 0.55 A      d) 0.60 A

162. The initial phase angle for  $i = 10 \sin \omega t + 8 \cos \omega t$  is

- a)  $\tan^{-1}\left(\frac{4}{5}\right)$       b)  $\tan^{-1}\left(\frac{5}{4}\right)$       c)  $\sin^{-1}\left(\frac{4}{5}\right)$       d)  $90^\circ$

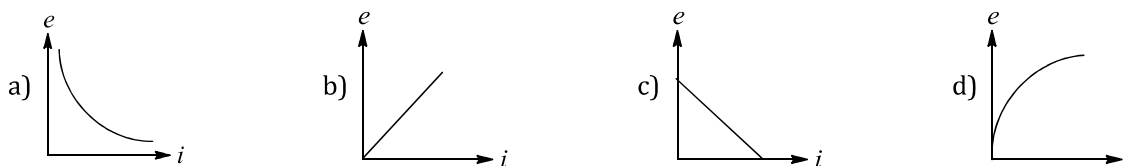163. In an  $L - R$  circuit shown in above figure switch  $S$  is closed at time  $t = 0$ . If  $e$  denotes the induced emf across inductor and  $i$ , the current in the circuit at any time  $t$ , then which of the following graphs, figure shows the variation of  $e$  with  $i$ ?



164. Same current is flowing in two alternating circuits. The first circuit contains only inductance and the other contains only a capacitor. If the frequency of the emf of AC is increased, the effect on the value of the current

- a) Increases in the first circuit and decreases in the other  
b) Increases in both the circuits  
c) Decreases in both the circuits  
d) Decreases in the first circuit and increases in the other

165. The number of turns of primary and secondary coils of a transformer is 5 and 10 respectively and mutual inductance of the transformer is 25 H. Now, number of turns in primary and secondary are made 10 and 5 respectively. Mutual inductance of transformer will be

- a) 25 H      b) 12.5 H      c) 50 H      d) 6.25 H

166. The armature of a shunt wound motor can with stand current up to 8A before it overheats and it damaged. If the armature resistance is  $0.5 \Omega$ , minimum back emf that must be motor is connected to a 120 V line is

- a) 120 V      b) 116 V      c) 124 V      d) 4 V

167. The current passing through a choke coil of 5 H is decreasing at the rate of  $2 \text{ As}^{-1}$ . The emf developed across the coil is

- a)  $-10 \text{ V}$       b)  $+10 \text{ V}$       c)  $2.5 \text{ V}$       d)  $-2.5 \text{ V}$

168. In an ac circuit, the current is given by  $i = 5 \sin\left(100t - \frac{\pi}{2}\right)$  and the ac potential is  $V = 200 \sin(100t)$  volt. Then the power consumption is

- a) 20 watts      b) 40 watts      c) 1000 watts      d) 0 watt

169. In a series circuit  $C = 2\mu\text{F}$ ,  $L = 1\text{mH}$  and  $R = 10\Omega$ . When the current in the circuit is maximum, at that time the ratio of the energies stored in the capacitor and the inductor will be

- a) 1 : 1      b) 1 : 2      c) 2 : 1      d) 1 : 5

170. In AC circuit a resistance of  $R \Omega$  is connected in series with an inductance  $L$ . If the phase difference between the current and voltage is  $45^\circ$ , the inductive reactance will be

- a)  $R/2$       b)  $R/4$       c)  $R$       d) None of the above

171. During a current change from 2 A to 4 A in 0.05 s, 8 V of emf is developed in a coil. The coefficient of self-induction is

- a) 0.1 H      b) 0.2 H      c) 0.4 H      d) 0.8 H

172. In a circuit, the current lags behind the voltage by a phase difference of  $\pi/2$ , the circuit will contain which of the following?

- a) Only  $R$       b) Only  $C$       c)  $R$  and  $C$       d) Only  $L$

173. In an ac circuit,  $V$  and  $I$  are given by

$V = 100 \sin(100t)$  volts,  $I = 100 \sin\left(100t + \frac{\pi}{3}\right)$  mA. The power dissipated in circuit is

- a)  $10^4$  watt      b) 10 watt      c) 2.5 watt      d) 5 watt


174. In a series resonant circuit, the AC voltage across resistance  $R$ , inductor  $L$  and capacitor  $C$  are 5 V, 10 V and 10 V respectively. The AC voltage applied to the current will be

- a) 10 V      b) 25 V      c) 5 V      d) 20 V

175. A  $10\ \Omega$  resistance,  $5\ \text{mH}$  coil and  $10\ \mu\text{F}$  capacitor are joined in series. When a suitable frequency alternating current source is joined to this combination, the circuit resonates. If the resistance is halved, the resonance frequency


- a) Is halved                      b) Is doubled                      c) Remains unchanged                      d) Is quadrupled

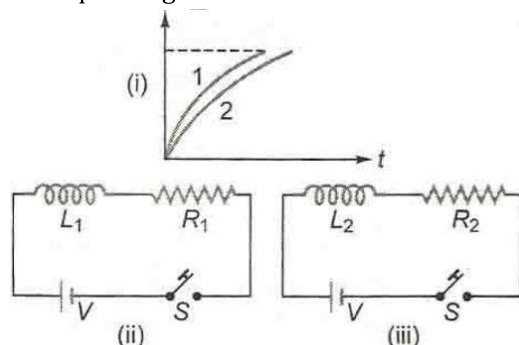176. Current growth in two  $L - R$  circuits (ii) and (iii) is as shown in figure (i). Let  $L_1, L_2, R_1$  and  $R_2$  be the corresponding values in two circuits. Then



- a)  $L_1 > L_2$                       b)  $L_1 < L_2$                       c)  $R_1 > R_2$                       d)  $R_1 = R_2$

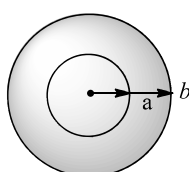177. Two concentric and coplanar circular coils have radii  $a$  and  $b$  as shown in figure. Resistance of the inner coil is  $R$ . Current in the other coil is increased from  $0$  to  $i$ , then the total charge circulating the inner coil is



- a)  $\frac{\mu_0 i a b}{2 R}$                       b)  $\frac{\mu_0 i a \pi b^2}{2 a b}$                       c)  $\frac{\mu_0 i b}{2 \pi R}$                       d)  $\frac{\mu_0 i a^2}{2 R b}$

178. Find the time required for a  $50\ \text{Hz}$  alternating current to become its value from zero to the rms value

- a)  $10.0\ \text{ms}$                       b)  $2.5\ \text{ms}$                       c)  $15.0\ \text{ms}$                       d)  $5.0\ \text{ms}$

179. A pure inductive coil of  $30\ \text{mH}$  is connected to an AC source of  $220\ \text{V}$ ,  $50\ \text{Hz}$ . The rms current in the coil is

- a)  $50.35\ \text{A}$                       b)  $23.4\ \text{A}$                       c)  $30.5\ \text{A}$                       d)  $12.3\ \text{A}$

180. In a circuit, the value of the alternating current is measured by hot wire ammeter as  $10\ \text{ampere}$ . Its peak value will be

- a)  $10\ \text{A}$                       b)  $20\ \text{A}$                       c)  $14.14\ \text{A}$                       d)  $7.07\ \text{A}$

181. The reactance of a coil when used in the domestic ac power supply ( $220\ \text{volts}$ ,  $50\ \text{cycles per second}$ ) is  $50\ \Omega$ . The inductance of the coil is nearly

- a)  $2.2\ \text{henry}$                       b)  $0.22\ \text{henry}$                       c)  $1.6\ \text{henry}$                       d)  $0.16\ \text{henry}$


182. In an ac circuit, peak value of voltage is  $423\ \text{volts}$ . Its effective voltage is

- a)  $400\ \text{volts}$                       b)  $323\ \text{volts}$                       c)  $300\ \text{volts}$                       d)  $340\ \text{volts}$

183. A circuit consists of an inductance of  $0.5\ \text{mH}$  and a capacitor of  $20\ \mu\text{F}$ . The frequency of the  $L - C$  oscillations is approximately

- a)  $400\ \text{Hz}$                       b)  $88\ \text{Hz}$                       c)  $1600\ \text{Hz}$                       d)  $2400\ \text{Hz}$

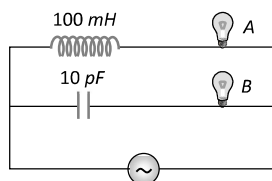184. If  $A$  and  $B$  are identical bulbs, which bulb glows brighter




- a)  $A$                       b)  $B$                       c) Both equally bright                      d) Cannot say

185. A coil of wire of certain radius has 100 turns and a self inductance of  $15\ \text{mH}$ . The self inductance of a second similar coil of 500 turns will be

- a) 75 mH                      b) 375 mH                      c) 15 mH                      d) None of these

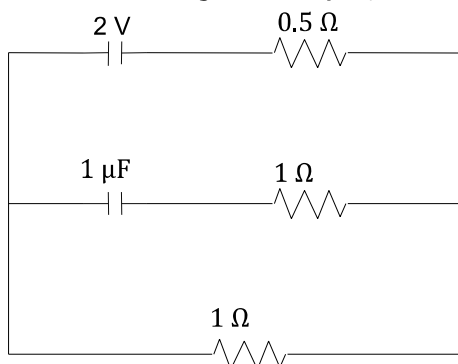186. What is the charge stored by  $1 \mu\text{F}$  as shown in the figure?




- a)  $2.33 \mu\text{C}$                       b)  $3.33 \mu\text{C}$                       c)  $1.33 \mu\text{C}$                       d)  $4.33 \mu\text{C}$

187. A pure inductor of  $25 \text{ mH}$  is connected to a source of  $220 \text{ V}$ . Given the frequency of the source as  $50 \text{ Hz}$ , the *rms* current in the circuit is

- a)  $7 \text{ A}$                       b)  $14 \text{ A}$                       c)  $28 \text{ A}$                       d)  $42 \text{ A}$

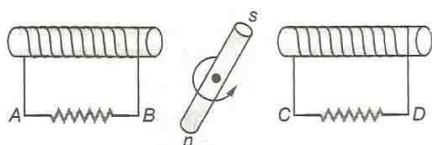188. The magnet in figure rotates as shown on a pivot through its center. At the instant shown, what are the directions of the induced currents.




- a)  $A$  to  $B$  and  $C$  to  $D$                       b)  $B$  to  $A$  and  $C$  to  $D$   
c)  $A$  to  $B$  and  $D$  to  $C$                       d)  $B$  to  $A$  and  $D$  to  $C$

189. A telephone wire of length  $200 \text{ km}$  has a capacitance of  $0.014 \mu\text{F}$  per  $\text{km}$ . If it carries an AC frequency  $5 \text{ kHz}$ , what should be the value of an inductor required to be connected in series so that the impedance of the circuit is minimum?

- a)  $0.35 \text{ mH}$                       b)  $3.5 \text{ mH}$                       c)  $2.5 \text{ mH}$                       d) zero

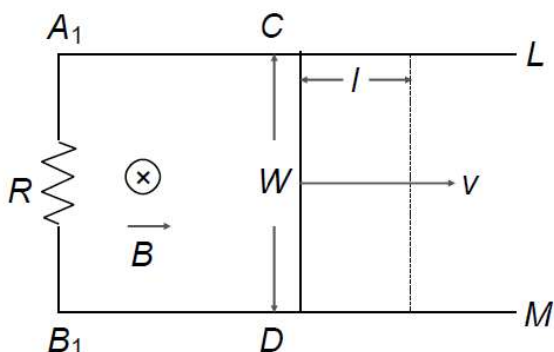190. Two parallel wires  $A_1L$  and  $B_1M$  placed at a distance  $w$  are connected by a resistor  $R$  and placed in a magnetic field  $B$  which is perpendicular to the plane containing the wires (see figure). Another wire  $CD$  now connects the two wires perpendicularly and made to slide with velocity  $v$  through distance  $L$ . The power developed is



- a)  $B \frac{lv}{R}$                       b)  $\frac{B^2 l^2 v^2}{R}$                       c)  $\frac{Bwv}{R}$                       d)  $\frac{B^2 w^2 v^2}{R}$

191. A  $12 \text{ ohm}$  resistor and a  $0.21 \text{ henry}$  inductor are connected in series to an ac source operating at  $20 \text{ volts}$ ,  $50 \text{ cycle/second}$ . The phase angle between the current and the source voltage is


- a)  $30^\circ$                       b)  $40^\circ$                       c)  $80^\circ$                       d)  $90^\circ$

192. The inductance of the oscillatory circuit of the radio station is  $10 \text{ mH}$  and its capacitance is  $0.25 \mu\text{F}$ . Taking the effect of resistance negligible, wavelength of the broadcasted waves will be (velocity of light =  $3.0 \times 10^8 \text{ m/s}$ )

$10^8 \text{ ms}^{-1}, \pi = 3.14$ )

- a)  $9.42 \times 10^4 \text{ m}$       b)  $18.8 \times 10^4 \text{ m}$       c)  $4.5 \times 10^4 \text{ m}$       d) None of these

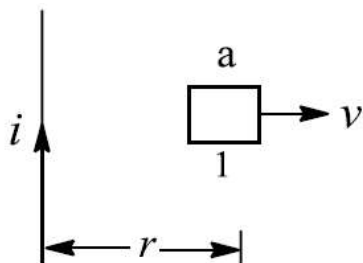193. A square loop of side  $a$  is placed in the same plane as a long straight wire carrying a current  $i$ . The centre of the loop is at a distance  $r$  from the wire, where  $r \gg a$ , figure. The loop is moved away from the wire with a constant velocity  $v$ . The induced emf in the loop is



- a)  $\frac{\mu_0 i a v}{2 \pi r}$       b)  $\frac{\mu_0 i a^3 v}{2 \pi r^3}$       c)  $\frac{\mu_0 i v}{2 \pi}$       d)  $\frac{\mu_0 i a^2 v}{2 \pi r^2}$

194. What is the r. m. s. value of an alternating current which when passed through a resistor produces heat which is thrice of that produced by a direct current of 2 amperes in the same resistor

- a) 6 amp      b) 2 amp      c) 3.46 amp      d) 0.66 amp

195. A 220 V, 50 Hz ac source is connected to an inductance of 0.2 H and a resistance of 20 ohm in series. What is the current in the circuit

- a) 10 A      b) 5 A      c) 33.3 A      d) 3.33 A


196. A coil of inductance  $L$  has an inductive reactance of  $X_L$  in an AC circuit in which the effective current is  $I$ . The coil is made from a super-conducting material and has no resistance. The rate at which power is dissipated in the coil is

- a) 0      b)  $IX_L$       c)  $I^2 X_L$       d)  $IX_L^2$

197. The resonant frequency of a circuit is  $f$ . If the capacitance is made 4 times the initial values, then the resonant frequency will become


- a)  $f/2$       b)  $2f$       c)  $f$       d)  $f/4$

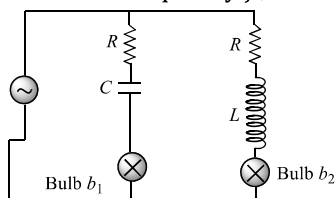198. Two identical incandescent light bulbs are connected as shown in figure. When the circuit is an AC voltage source of frequency  $f$ , which of the following observation will be correct




- a) Both bulbs will glow alternatively  
b) Both bulbs will glow with same brightness provided  $f = \frac{1}{2\pi} \sqrt{1/LC}$   
c) Bulb  $b_1$  will light up initially and goes off, bulb  $b_2$  will be ON constantly  
d) Bulb  $b_1$  will blink and bulb  $b_2$  will be ON constantly

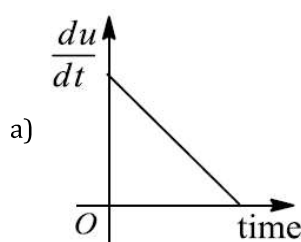
199. In an  $L - R$  circuit to a battery, the rate at which energy is stored in the inductor is plotted against time during the growth of current in the circuit. Which of the following, figure best represents the resulting curve?






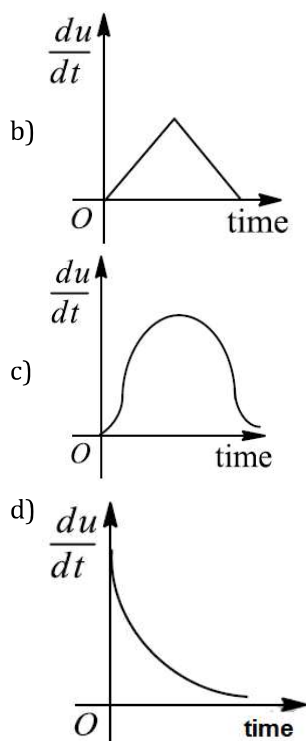

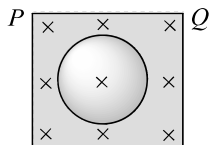200. A vertical ring of radius  $r$  and resistance  $R$  falls vertically. It is in contact with two vertical rails which are joined at the top, figure. The rails are without friction and resistance. There is a horizontal uniform magnetic field of magnitude  $B$  perpendicular to the plane of the ring and the rails. When the speed of the ring is  $v$ , the current in the section  $PQ$  is



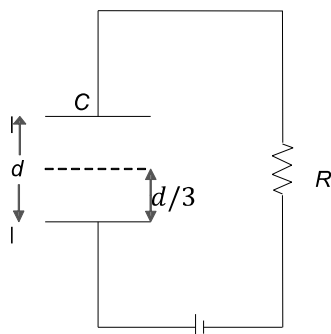- a) Zero                      b)  $\frac{2 Rrv}{R}$                       c)  $\frac{4 Rrv}{R}$                       d)  $\frac{8 Brv}{R}$
201. A circuit has a resistance of  $11\Omega$ , an inductive reactance of  $25\Omega$  and a capacitive reactance of  $18\Omega$ . It is connected to an ac source of  $260V$  and  $50Hz$ . The current through the circuit (in amperes) is
- a) 11                      b) 15                      c) 18                      d) 20
202. If instantaneous current is given by  $i = 4 \cos(\omega t + \phi)$  amperes, then the r.m.s value of current is
- a) 4 amperes                      b)  $2\sqrt{2}$  amperes                      c)  $4\sqrt{2}$  amperes                      d) Zero amperes
203. A parallel plate capacitor  $C$  with plates of unit area and separation  $d$  is filled with a liquid of dielectric constant  $K=2$ . The level of liquid is  $\frac{d}{3}$  initially. Suppose the liquid level decreases at a constant speed  $v$ , the time constant as a function of time  $t$  is.



- a)  $\frac{6\epsilon_0 R}{5d + 3vt}$                       b)  $\frac{(15d + 9vt)\epsilon_0 R}{2d^2 - 3dvt - 9v^2t^2}$                       c)  $\frac{6\epsilon_0 R}{5d - 3vt}$                       d)  $\frac{(15d - 9vt)\epsilon_0 R}{2d^2 + 3dvt - 9v^2t^2}$




204. Radio frequency choke uses core of

- a) Air                                      b) Iron                                      c) Air and iron                                      d) None of these

205. In a  $L - R$  circuit of 3 mH inductance and  $4 \Omega$  resistance, emf  $E = 4 \cos 1000t$  V is applied. The amplitude of emf is

- a) 0.8 A                                      b)  $\frac{4}{7}$  A                                      c) 1.0 A                                      d)  $\frac{4}{\sqrt{7}}$  A

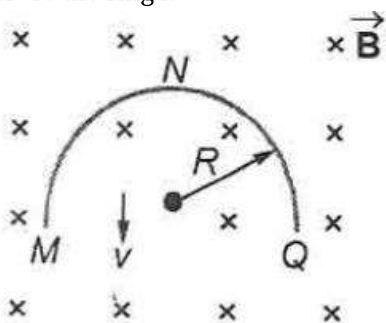206. A thin semicircular conducting ring of radius  $R$  is falling with its plane vertical in a horizontal magnetic induction  $\vec{B}$ , figure. At the position  $MNQ$ , the speed of the ring is  $v$ . The potential difference developed across the ring is



- a) Zero  
b)  $\frac{1}{2} B v \pi R^2$ , and  $M$  is at a higher potential  
c)  $\pi R B v$ , and  $Q$  is at a higher potential  
d)  $2 R B v$ , and  $Q$  is at a higher potential

207. When a coil carrying a steady current is short circuited, the current in it, decreases  $\eta$  time in time  $t_0$ . The time constant of the circuit is

- a)  $\frac{t_0}{\ln \eta}$                                       b)  $\frac{t_0}{\eta - 1}$                                       c)  $t_0 \ln \eta$                                       d)  $\frac{t_0}{\eta}$

208. An inductor of 2 H and a resistance of  $10 \Omega$  are connected in series with a battery of 5 V. the initial rate of change of current is

- a)  $0.5 \text{ As}^{-1}$                                       b)  $2.0 \text{ As}^{-1}$                                       c)  $2.5 \text{ As}^{-1}$                                       d)  $0.25 \text{ As}^{-1}$

209. What is the average value of the AC voltage over one complete cycle?

- a) Zero                                      b)  $V_{\max}$                                       c)  $\frac{2V_{\max}}{\pi}$                                       d)  $\frac{V_{\max}}{2}$

210. Power delivered by the source of the circuit becomes maximum, when

- a)  $\omega L = \omega C$                                       b)  $\omega L = \frac{1}{\omega C}$                                       c)  $\omega L = -\left(\frac{1}{\omega C}\right)^2$                                       d)  $\omega L = \sqrt{\omega C}$

211. What is the approximate peak value of an alternating current producing four times the heat produced per second by a steady current of 2.0 A in a resistor

- a) 2.8 A                                      b) 4.0 A                                      c) 5.6 A                                      d) 8.0 A

212. In an AC circuit the emf( $e$ ) and the current ( $i$ ) at any instant are given respectively by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of AC is

- a)  $\frac{E_0 I_0}{2}$                                       b)  $\frac{E_0 I_0}{2} \sin \phi$                                       c)  $\frac{E_0 I_0}{2} \cos \phi$                                       d)  $E_0 I_0$


213. The frequency of ac mains in India is

- a) 30 c/s or Hz                                      b) 50 c/s or Hz                                      c) 60 c/s or Hz                                      d) 120 c/s or Hz





214. An air cored coil has a self-inductance of 0.1 H. A soft iron core of relative permeability 100 is  $1/10$  th. The value of self-inductance now becomes

- a) 1 mH                                      b) 10 mH                                      c) 0.4 H                                      d) 0.8 H

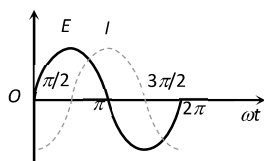215. If  $E_0$  represents the peak value of the voltage in an ac circuit, the *r.m.s* value of the voltage will be  
 a)  $\frac{E_0}{\pi}$                       b)  $\frac{E_0}{2}$                       c)  $\frac{E_0}{\sqrt{\pi}}$                       d)  $\frac{E_0}{\sqrt{2}}$
216. The capacity of a pure capacitor is 1 *farad*. In dc circuits, its effective resistance will be  
 a) Zero                      b) Infinite                      c) 1 *ohm*                      d) 1/2 *ohm*
217. If an ac main supply is given to be 220 V. What would be the average *e.m.f.* during a positive half cycle  
 a) 198V                      b) 386V                      c) 256V                      d) None of these
218. The variation of the instantaneous current ( $I$ ) and the instantaneous *emf* ( $E$ ) in a circuit is as shown in fig. Which of the following statements is correct




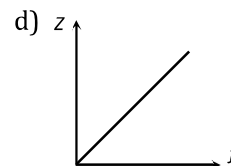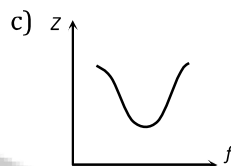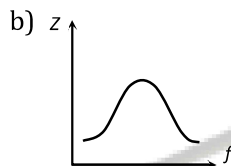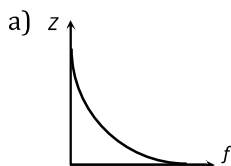- a) The voltage lags behind the current by  $\pi/2$                       b) The voltage leads the current by  $\pi/2$   
 c) The voltage and the current are in phase                      d) The voltage leads the current by  $\pi$
219. Which one of the following curves represents the variation of impedance ( $Z$ ) with frequency  $f$  in series *LCR* circuit







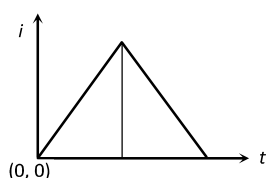220. An alternating current source of frequency 100 Hz is joined to a combination of a resistance, a capacitance and a coil in series. The potential difference across the coil, the resistance and the capacitor is 46, 8 and 40 *volt* respectively. The electromotive force of alternating current source in *volt* is  
 a) 94                      b) 14                      c) 10                      d) 76
221. The voltage of an ac source varies with time according to the equation  $V = 100 \sin 100\pi t \cos 100\pi t$  where  $t$  is in second and  $V$  is in volts. Then  
 a) The peak voltage of the source is 100 *volts*  
 b) The peak voltage of the source is 50 *volts*  
 c) The peak voltage of the source is  $100/\sqrt{2}$  *volts*  
 d) The frequency of the source is 50 Hz
222. A resistance  $R$ , inductance  $L$  and capacitor  $C$  are connected in series to an oscillator of frequency  $f$ . If resonant frequency is  $f_r$ , then current will lag the voltage when  
 a)  $f = 0$                       b)  $f < f_r$                       c)  $f = f_r$                       d)  $f > f_r$
223. There is a  $5\Omega$  resistance in an ac, circuit. Inductance of 0.1H is connected with it in series. If equation of ac *e.m.f.* is  $5 \sin 50t$ , then the phase difference between current and *e.m.f.* is  
 a)  $\frac{\pi}{2}$                       b)  $\frac{\pi}{6}$                       c)  $\frac{\pi}{4}$                       d) 0
224. In an AC circuit the voltage applied is  $E = E_0 \sin \omega t$ . The resulting current in the circuit is  $I = I_0 \sin \left( \omega t - \frac{\pi}{2} \right)$ . The power consumption in the circuit is given by  
 a)  $P = \frac{E_0 I_0}{\sqrt{2}}$                       b)  $P = \text{zero}$                       c)  $P = \frac{E_0 I_0}{2}$                       d)  $P = \sqrt{2} E_0 I_0$
225. The phase difference between the voltage and the current in an ac circuit is  $\pi/4$ . If the frequency is 50 Hz then this phase difference will be equivalent to a time of  
 a) 0.02 s                      b) 0.25 s                      c) 2.5 ms                      d) 25 ms
226. A uniformly wound solenoidal coil of self inductance  $1.8 \times 10^{-4}$  H and resistance 6  $\Omega$  is broken up into two identical coils. These identical coils are then connected in parallel across a 12 V battery of negligible

- resistance. The time constant of the current in the circuit and the steady state current through battery is  
a)  $3 \times 10^{-5}$  s, 8 A      b)  $1.5 \times 10^{-5}$  s, 8 A      c)  $0.75 \times 10^{-4}$  s, 4 A      d)  $6 \times 10^{-5}$  s, 2 A
227. An ac voltage is applied to a resistance  $R$  and inductor  $L$  in series. If  $R$  and the inductive reactance are both equal to  $3\Omega$ , the phase difference between the applied voltage and the current in the circuit is  
a) Zero      b)  $\pi/6$       c)  $\pi/4$       d)  $\pi/2$
228. An inductance of  $1\text{ mH}$  a condenser of  $10\text{ }\mu\text{F}$  and a resistance of  $50\text{ }\Omega$  are connected in series. The reactances of inductor and condensers are same. The reactance of either of them will be  
a)  $100\text{ }\Omega$       b)  $30\text{ }\Omega$       c)  $3.2\text{ }\Omega$       d)  $10\text{ }\Omega$
229. In a series  $L - C - R$  circuit the frequency of a  $10\text{ V}$  AC voltage source is adjusted in such a fashion that the reactance of the inductor measures  $15\text{ }\Omega$  and that of the capacitor  $11\text{ }\Omega$ . If  $R = 3\text{ }\Omega$ , the potential difference across the series combination of  $L$  and  $C$  will be  
a)  $8\text{ V}$       b)  $10\text{ V}$       c)  $22\text{ V}$       d)  $52\text{ V}$
230. The current ' $i$ ' in an inductance coil varies with time ' $t$ ' according to following graph




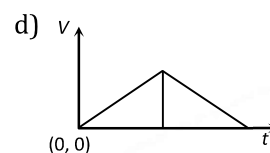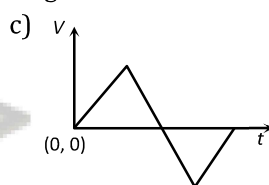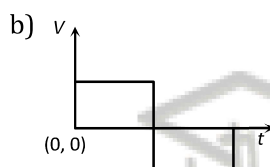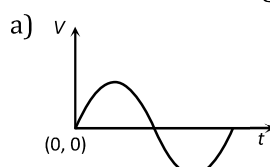Which of the following plots shows the variation of voltage in the coil



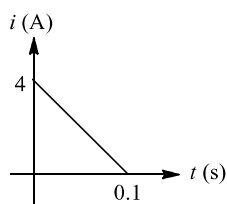231. For a coil having  $L = 2\text{ mH}$ , current flows at the rate of  $10^3\text{ As}^{-1}$ . The emf induced is  
a)  $2\text{ V}$       b)  $1\text{ V}$       c)  $4\text{ V}$       d)  $3\text{ V}$
232. In a series resonant  $R-L-C$  circuit, the voltage across  $R$  is  $100\text{ V}$  and the value of  $R = 1000\text{ }\Omega$ . The capacitance of the capacitor is  $2 \times 10^{-6}\text{ F}$ ; angular frequency of AC is  $200\text{ rad s}^{-1}$ . Then the potential difference across the inductance coil is  
a)  $100\text{ V}$       b)  $40\text{ V}$       c)  $250\text{ V}$       d)  $400\text{ V}$
233. A group of electric lamps having a total power rating of  $1000\text{ watt}$  is supplied by an ac voltage  $E = 200 \sin(310t + 60^\circ)$ . Then the r. m. s. value of the circuit current is  
a)  $10\text{ A}$       b)  $10\sqrt{2}\text{ A}$       c)  $20\text{ A}$       d)  $20\sqrt{2}\text{ A}$
234. When the rate of change of current is unity, induced emf is equal to  
a) Thickness of coil      b) Number of turns in coil      c) Coefficient of self-induction      d) Total flux linked with coil
235. The induced emf of a generator when the flux of poles is doubled and speed is doubled  
a) Becomes half      b) Remains same  
c) Becomes double      d) Becomes 4 times
236. In the non-resonant circuit, what will be the nature of the circuit for frequencies higher than the resonant frequency  
a) Resistive      b) Capacitive      c) Inductive      d) None of the above
237.  $\frac{R}{L}$  has the dimensions to  
a) Time      b) Mass      c) Length      d) Frequency
238. If  $E = 100 \sin(100t)$  volt and  $I = 100 \sin\left(100t + \frac{\pi}{3}\right)\text{ mA}$  are the instantaneous values of voltage and current, then the r. m. s. values of voltage and current are respectively  
a)  $70.7\text{ V}, 70.7\text{ mA}$       b)  $70.7\text{ V}, 70.7\text{ A}$       c)  $141.4\text{ V}, 141.4\text{ mA}$       d)  $141.4\text{ V}, 141.4\text{ A}$
239. Some magnetic flux is changed from a coil of resistance  $110\text{ }\Omega$ . As a result, an induced current is developed

in it, which varies with time as shown in figure. The magnitude of change in flux through the coil in weber is




- a) 4                                      b) 8                                      c) 2                                      d) 6

240. The armature of a DC motor has a resistance of  $20\ \Omega$ . It draws a current of  $1.5\text{ A}$  when run by  $220\text{ V DC}$ . The value of peak emf induced in it will be

- a)  $150\text{ V}$                                       b)  $170\text{ V}$                                       c)  $190\text{ V}$                                       d)  $180\text{ V}$

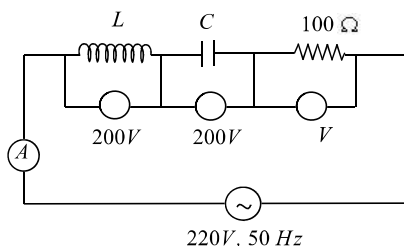241. The readings of ammeter and voltmeter in the following circuit are respectively



- a)  $2\text{ A}, 200\text{ V}$                                       b)  $1.5\text{ A}, 100\text{ V}$                                       c)  $2.7\text{ A}, 220\text{ V}$                                       d)  $2.2\text{ A}, 220\text{ V}$

242. In  $L - C - R$  series circuit the resonance condition in terms of capacitive reactance ( $X_C$ ) and inductive reactance ( $X_L$ ) is

- a)  $X_C + X_L = 0$                                       b)  $X_C = 0$                                       c)  $X_L = 0$                                       d)  $X_C - X_L = 0$

243. The power is transmitted from a power house on high voltage ac because

- a) Electric current travels faster at higher volts  
b) It is more economical due to less power wastage  
c) It is difficult to generate power at low voltage  
d) Changes of stealing transmission lines are minimized

244. The frequency of an alternating voltage is  $50\text{ cycles/sec}$  and its amplitude is  $120\text{ V}$ . Then the r.m.s. value of voltage is

- a)  $101.3\text{ V}$                                       b)  $84.8\text{ V}$                                       c)  $70.7\text{ V}$                                       d)  $56.5\text{ V}$

245.  $220\text{ V}, 50\text{ Hz AC}$  is applied to a resistor. The instantaneous value of voltage is

- a)  $220\sqrt{2} \sin 100\pi t$                                       b)  $220 \sin 100\pi t$                                       c)  $220\sqrt{2} \sin 50\pi t$                                       d)  $220 \sin 50\pi t$


246.  $L, C$  and  $R$  represent physical quantities inductance capacitance and resistance respectively. The combination representing dimension of frequency is

- a)  $LC$                                       b)  $(LC)^{-1/2}$                                       c)  $\left(\frac{L}{C}\right)^{-1/2}$                                       d)  $\frac{C}{L}$

247. For series  $LCR$  circuit, wrong statement is

- a) Applied e.m.f. and potential difference across resistance are in same phase  
b) Applied e.m.f. and potential difference at inductor coil have phase difference of  $\pi/2$   
c) Potential difference at capacitor and inductor have phase difference of  $\pi/2$   
d) Potential difference across resistance and capacitor have phase difference of  $\pi/2$

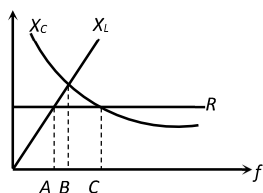248. The figure shows variation of  $R, X_L$  and  $X_C$  with frequency  $f$  in a series  $L, C, R$  circuit. Then for what frequency  $f$  in a series  $L, C, R$  circuit. Then for what frequency point, the circuit is inductive




- a) A                                      b) B                                      c) C                                      d) All points

249. Current in the LCR circuit becomes extremely large when

- a) Frequency of AC supply is increased  
b) Frequency of AC supply is decreased  
c) Inductive reactance becomes equal to capacitive reactance  
d) Inductance becomes equal to capacitance

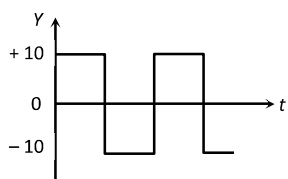250. The r. m. s. voltage of the wave form shown is




- a) 10 V                                      b) 7 V                                      c) 6.37 V                                      d) None of these

251. Two coils A and B have 200 and 400 turns respectively. A current of 1 A in coil A causes a flux per turn of  $10^{-3}$  Wb to link with A and a flux per turn of  $0.8 \times 10^{-3}$  Wb through B. The ratio of mutual inductance of A and B is

- a) 0.625                                      b) 1.25                                      c) 1.5                                      d) 1.625

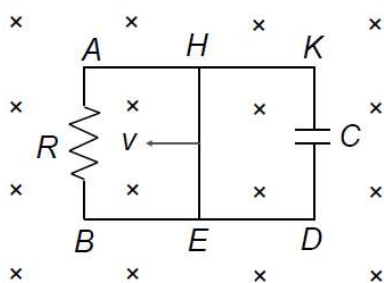252. In the circuit shown in figure, a conducting wire HE is moved with a constant speed  $v$  towards left. The complete circuit is placed in a uniform magnetic field  $\vec{B}$  perpendicular to the plane of circuit inwards. The current in HKDE is




- a) Anti-clock-wise                      b) Clock-wise                      c) Alternating                      d) Zero

253. A circuit area is  $0.01 \text{ m}^2$  is kept inside a magnetic field which is normal to its plane. The magnetic field changes from 2 T to 1 T in 1 millisecond. If the resistance of the circuit is  $2 \Omega$ . The amount of heat evolved is


- a) 0.05 J                                      b) 50 J                                      c) 0.50 J                                      d) 500 J

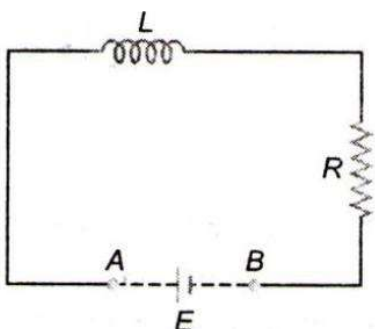254. An inductor ( $L = 100 \text{ mH}$ ), a resistor ( $R = 100 \Omega$ ) and a battery ( $E = 100 \text{ V}$ ) are initially connected in series as shown in figure. After a long time the battery is disconnected after short circuiting the points A and B.


The current in the circuit 1 ms after the short circuit is



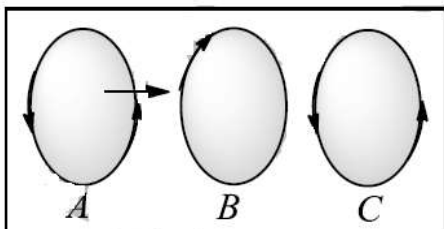- a)  $1/e \text{ A}$       b)  $e \text{ A}$       c)  $0.1 \text{ A}$       d)  $1 \text{ A}$
255. The ratio of peak value and *r. m. s.* value of an alternating current is  
 a) 1      b)  $\frac{1}{2}$       c)  $\sqrt{2}$       d)  $1/\sqrt{2}$
256. One  $10 \text{ V}$ ,  $60 \text{ W}$  bulb is to be connected to  $100 \text{ V}$  line. The required induction coil has self inductance of value ( $f = 50 \text{ Hz}$ )  
 a)  $0.052 \text{ H}$       b)  $2.42 \text{ H}$       c)  $16.2 \text{ mH}$       d)  $1.62 \text{ mH}$
257. In  $L - C - R$  circuit if resistance increases, quality factor  
 a) Increases finitely      b) Decreases finitely      c) Remains constant      d) None of the above
258. An inductance of  $\left(\frac{200}{\pi}\right) \text{ mH}$ , a capacitance of  $\left(\frac{10^{-3}}{\pi}\right) \text{ F}$  and a resistance of  $10 \Omega$  are connected in series with an AC source  $220 \text{ V}$ ,  $50 \text{ Hz}$ . The phase angle of the circuit is  
 a)  $\frac{\pi}{6}$       b)  $\frac{\pi}{4}$       c)  $\frac{\pi}{2}$       d)  $\frac{\pi}{3}$
259. Which of the following statement is incorrect?  
 a) In a  $L - C - R$  series AC circuit, as the frequency of the source increases, the impedance of the circuit first decreases and then increases  
 b) If the net reactance of an  $L - C - R$  series AC circuit is same as its resistance, then the current lags behind the voltage by  $45^\circ$   
 c) At resonance, the impedance of an AC circuit becomes purely resistive.  
 d) Below resonance, voltage leads the current while above it, current leads the voltage
260. Power factor is maximum in an  $LCR$  circuit when  
 a)  $X_L = X_C$       b)  $R = 0$       c)  $X_L = 0$       d)  $X_C = 0$
261. A  $280 \text{ ohm}$  electric bulb is connected to  $200 \text{ V}$  electric line. The peak value of current in the bulb will be  
 a) About one ampere      b) Zero      c) About two ampere      d) About four ampere
262. Three identical coils  $A$ ,  $B$  and  $C$  are placed with their planes parallel to one another. Coils  $A$  and  $C$  carry currents as shown in figure. Coils  $B$  and  $C$  are fixed in position and coil  $A$  is moved towards  $B$ . Then, current induced in  $B$  is in




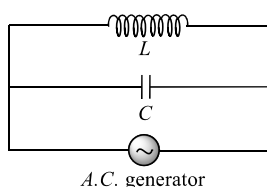- a) Clock-wise current  
 b) Anti-clock-wise current  
 c) No current is induced in  $B$   
 d) Current is induced only when both coils move
263. In the alternating current shown in the figure, the currents through inductor and capacitor are  $1.2 \text{ amp}$  and  $1.0 \text{ amp}$  respectively. The current drawn from the generator is



- a) 0.4 amp                      b) 0.2 amp                      c) 1.0 amp                      d) 1.2 amp

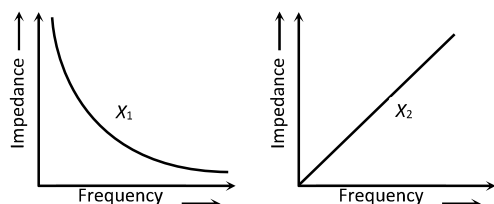264. The graphs given below depict the dependence of two reactive impedances  $X_1$  and  $X_2$  on the frequency of the alternating e.m.f. applied individually to them. We can then say that



- a)  $X_1$  is an inductor and  $X_2$  is a capacitor                      b)  $X_1$  is a resistor and  $X_2$  is a capacitor  
c)  $X_1$  is a capacitor and  $X_2$  is an inductor                      d)  $X_1$  is an inductor and  $X_2$  is a resistor

265. The resistance of an  $R$ - $L$  circuit is  $10\ \Omega$ . An emf  $E_0$  applied across the circuit at  $\omega = 20\ \text{rad s}^{-1}$ . If the current in the circuit is  $\frac{i_0}{\sqrt{2}}$  what is the value of  $L$ ?

- a) 0.5 H                      b) 2.25 H                      c) 3.9 H                      d) 1.0 H

266.  $L$ ,  $C$  and  $R$  denote inductance, capacitance and resistance respectively. Pick out the combination which does not have the dimensions of frequency

- a)  $\frac{1}{RC}$                       b)  $\frac{R}{L}$                       c)  $\frac{1}{\sqrt{LC}}$                       d)  $\frac{C}{L}$

267. In a series resonant  $L$  -  $C$  -  $R$  circuit, the voltage across  $R$  is 100 V and  $R = 1\ \text{k}\Omega$  with  $C = 2\ \mu\text{F}$ . The resonant frequency  $\omega$  is  $200\ \text{rads}^{-1}$ . At resonance the voltage across  $L$  is

- a)  $2.5 \times 10^{-2}\ \text{V}$                       b) 40 V                      c) 250 V                      d)  $4 \times 10^{-3}\ \text{V}$

268. In an electrical circuit  $R$ ,  $L$ ,  $C$  and an a.c. voltage source are all connected in series. When  $L$  is removed from the circuit, the phase difference between the voltage and the current in the circuit is  $\pi/3$ . If instead,  $C$  is removed from the circuit, the phase difference is again  $\pi/3$ . The power factor of the circuit is

- a)  $1/2$                       b)  $1/\sqrt{2}$                       c) 1                      d)  $\sqrt{3}/2$


269. The phase difference between the alternating current and emf is  $\pi/2$ . Which of the following cannot be the constituent of the circuit?

- a)  $C$  alone                      b)  $R, L$                       c)  $L, C$                       d)  $L$  alone

270. The phase angle between e.m.f. and current in  $LCR$  series as circuit is

- a) 0 to  $\frac{\pi}{2}$                       b)  $\frac{\pi}{4}$                       c)  $\frac{\pi}{2}$                       d)  $\pi$

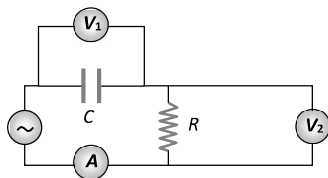271. The diagram shows a capacitor  $C$  and a resistor  $R$  connected in series to an ac source.  $V_1$  and  $V_2$  are voltmeters and  $A$  is an ammeter



Consider the following statements

I. Readings in  $A$  are always in phase

II. Reading in  $V_1$  is ahead in phase with reading in  $V_2$

III. Reading in  $A$  and  $V_1$  are always in phase. Which of these statements are/is correct

- a) I only                      b) II only                      c) I and II only                      d) II and III only

272. An alternating current of rms value 10 A is passed through a  $12\ \Omega$  resistor. The maximum potential



difference across the resistor is

- a) 20V                      b) 90V                      c) 169.68 V                      d) None of these


273. The current  $i$  passed in any instrument in an AC circuit is  $i = 2 \sin \omega t$  A and potential difference applied is given by  $V = 5 \cos \omega t$  V. Power loss in the instrument is

- a) 10 W                      b) 5 W                      c) Zero W                      d) 20 W

274. In a series  $L - C - R$  circuit, resistance  $R = 10 \Omega$  and the impedance  $Z = 10 \Omega$ . The phase difference between the current and the voltage is

- a)  $0^\circ$                       b)  $30^\circ$                       c)  $45^\circ$                       d)  $60^\circ$

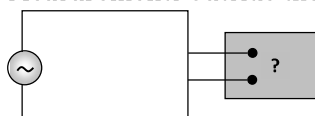275. Following figure shows an ac generator connected to a "block box" through a pair of terminals. The box contains possible  $R, L, C$  or their combination, whose elements and arrangements are not known to us. Measurements outside the box reveals t



$$e = 75 \sin(\sin \omega t) \text{ volt,}$$

$$i = 1.5 \sin(\omega t + 45^\circ) \text{ amp.}$$


The wrong statement is

- a) There must be a capacitor in the box                      b) There must be an inductor in the box  
c) There must be a resistance in the box                      d) The power factor is 0.707

276. A capacitor and an inductance coil are connected in separate AC circuits with a bulb glowing in both the circuits. The bulb glows more brightly when

- a) An iron rod is introduced into the inductance coil  
b) The number of turns in the inductance coil is increased  
c) Separation between the plates of the capacitor is increased  
d) A dielectric is introduced into the gap between the plates of the capacitor

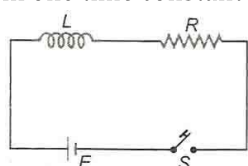277. In the circuit shown in figure switch  $S$  is closed at time  $t = 0$ . The charge which passes through the battery in one time constant is




- a)  $\frac{EL}{eR^2}$                       b)  $\frac{eL}{ER}$                       c)  $\frac{eR^2E}{L}$                       d)  $E \left( \frac{L}{R} \right)$

278. A coil of inductance 0.2 H and 1.0 W resistance is connected to a 90 V source. At what rate will the current in the coil grow at the instant the coil is connected to the source?

- a)  $450 \text{ As}^{-1}$                       b)  $4.5 \text{ As}^{-1}$                       c)  $45 \text{ As}^{-1}$                       d)  $0.45 \text{ As}^{-1}$

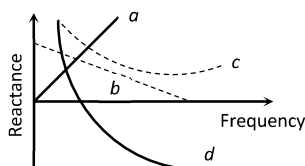279. Which of the following plots may represent the reactance of a series  $LC$  combination




- a) a                      b) b                      c) c                      d) d

280. A coil of inductive reactance  $31\Omega$  has a resistance of  $8\Omega$ . It is placed in series with a condenser of capacitive reactance  $25\Omega$ . The combination is connected to an a.c. source of 110 volt. The power factor of the circuit is

- a) 0.80                      b) 0.33                      c) 0.56                      d) 0.64

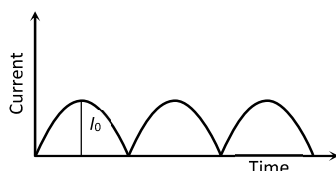281. The output current versus time curve of a rectifier is shown in the figure. The average value of output current in this case is





- a) 0                      b)  $\frac{I_0}{2}$                       c)  $\frac{2I_0}{\pi}$                       d)  $I_0$


282. A  $LCR$  series  $A.C.$  circuit is tuned to resonance. The impedance of the circuit is now

- a)  $R$                       b)  $\left[ R^2 + \left( \frac{1}{\omega C} - \omega L \right)^2 \right]^{1/2}$   
 c)  $\left[ R^2 + (\omega L)^2 + \left( \frac{1}{\omega C} \right)^2 \right]^{1/2}$                       d)  $\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{1/2}$

283. A transistor-oscillator using a resonant circuit with an inductor  $L$  (of negligible resistance) and a capacitor  $C$  in series produce oscillation of frequency  $f$ . If  $L$  is doubled and  $C$  is changed to  $4C$ , the frequency will be

- a)  $f/2\sqrt{2}$                       b)  $f/2$                       c)  $f/4$                       d)  $8f$

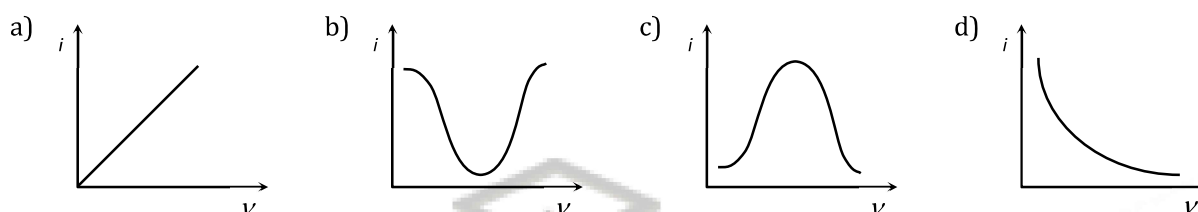284. The  $i - v$  curve for anti-resonant circuit is



285. Consider a short magnetic dipole of magnetic length 10 cm. Its geometric length is

- a) 12 cm                      b) 5                      c) 3                      d) 4

286. Two electric bulbs marked  $25W - 220V$  and  $100W - 220V$  are connected in series to a  $440V$  supply.


Which of the bulbs will fuse

- a) Both                      b) 100 W                      c) 25 W                      d) Neither

287. An ideal coil of 10 H is connected in series with a resistance of  $5 \Omega$  and a battery of 5 V. 2s after the connection is made, the current flowing (in ampere) in the circuit is

- a)  $(1 - e)$                       b)  $e$                       c)  $e^{-1}$                       d)  $(1 - e^{-1})$

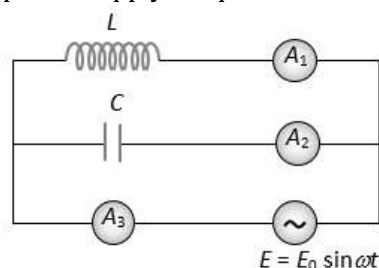288. An inductor  $L$  and a capacitor  $C$  are connected in the circuit as shown in the figure. The frequency of the power supply is equal to the resonant frequency of the circuit. Which ammeter will read zero ampere





- a)  $A_1$   
 b)  $A_2$   
 c)  $A_3$   
 d) None of these

289. The power factor of an AC circuit having resistance  $R$  and inductance  $L$  (connected in series) and an angular velocity  $\omega$  is


- a)  $R/\omega L$                       b)  $R/(R^2 + \omega^2 L^2)^{1/2}$                       c)  $\omega L/R$                       d)  $R/(R^2 - \omega^2 L^2)^{1/2}$

290. If coefficient of self induction of a coil is 1 H, an emf of 1 V is induced, if


- a) Current flowing is 1 A                      b) Current variation rate is  $1 \text{ As}^{-1}$

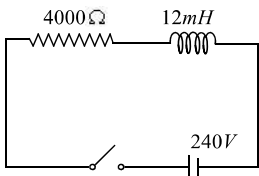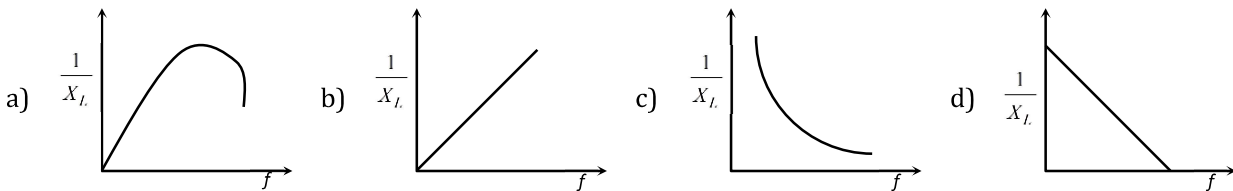- c) Current of 1 A flows for one sec  
d) None of the above
291. The power loss in AC circuit will be minimum when  
a) Resistance is high, inductance is high  
b) Resistance is high, inductance is low  
c) Resistance is low, inductance is low  
d) None of the above
292. What is the average power dissipation in an ideal capacitor in AC circuit?  
a)  $2CV^2$   
b)  $\frac{1}{2}CV^2$   
c) Zero  
d)  $CV^2$
293. The instantaneous voltage through a device of impedance  $20\ \Omega$  is  $e = 80 \sin 100\ \pi t$ . The effective value of the current is  
a) 3 A  
b) 2.828 A  
c) 1.732 A  
d) 4 A
294. In a series LCR circuit, operated with an ac of angular frequency  $\omega$ , the total impedance is  
a)  $[R^2 + (L\omega - C\omega)^2]^{1/2}$   
b)  $\left[R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2\right]^{1/2}$   
c)  $\left[R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2\right]^{-1/2}$   
d)  $\left[(R\omega)^2 + \left(L\omega - \frac{1}{C\omega}\right)^2\right]^{1/2}$
295. Two coils have mutual inductance 0.005 H. The current changes in the first coil according to equation  $i = i_0 \sin \omega t$  where  $i_0 = 10\text{ A}$  and  $\omega = 100\pi\text{ rads}^{-1}$ . The maximum value of emf in second coil is  
a)  $2\pi$   
b)  $5\pi$   
c)  $\pi$   
d)  $4\pi$
296. In the inductive circuit given in the figure, the current rises after the switch is closed. At instant when the current is 15 mA, then potential difference across the inductor will be
- 
- a) Zero  
b) 240V  
c) 180V  
d) 60V
297. An e.m.f.  $E = 4 \cos(1000t)$  volt is applied to an LR-circuit of inductance 3 mH and resistance 4 ohms. The amplitude of current in the circuit is  
a)  $\frac{4}{\sqrt{7}}\text{ A}$   
b) 1.0 A  
c)  $\frac{4}{7}\text{ A}$   
d) 0.8 A
298. An inductance 1 H is connected in series with an AC source of 220 V and 50 Hz. The inductive reactance (in ohm) is  
a)  $2\pi$   
b)  $50\pi$   
c)  $100\pi$   
d)  $1000\pi$
299. In pure inductive circuit, the curves between frequency  $f$  and reciprocal of inductive reactance  $1/X_L$  is
- 
- a)  $\frac{1}{X_L}$   
b)  $\frac{1}{X_L}$   
c)  $\frac{1}{X_L}$   
d)  $\frac{1}{X_L}$
300. The maximum voltage in DC circuit is 282V. The effective voltage in AC circuit will be  
a) 200 V  
b) 300 V  
c) 400 V  
d) 564 V
301. An irregular closed loop carrying a current has a shape such that the entire loop cannot lie in a single plane. If this is placed in a uniform magnetic field, the force acting on the loop  
a) Must be zero  
b) Can never be zero  
c) May be zero  
d) Will be zero only for one particular direction of the magnetic field
302. A 50 V AC is applied across an R-C (series) network. The rms voltage across the resistance is 40 V, then the potential across the capacitance would be

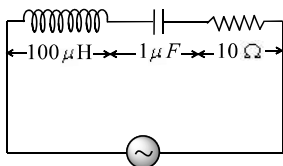- a) 10 V                      b) 20 V                      c) 30 V                      d) 40 V
303. A resistor  $30\ \Omega$ , inductor of reactance  $10\ \Omega$  and capacitor of reactance  $10\ \Omega$  are connected in series to an AC voltage source  $e = 300\sqrt{2} \sin(\omega t)$ . The current in the circuit is
- a)  $10\sqrt{2}\text{ A}$                       b) 10 A                      c)  $30\sqrt{11}\text{ A}$                       d)  $30/\sqrt{11}\text{ A}$
304. The number of turns in a secondary coil is twice the number of turns in primary. A leclanche cell of 1.5 V is connected across the primary. The voltage across secondary is
- a) 1.5 V                      b) 3.0 V                      c) 240 V                      d) Zero
305. If an alternating voltage is represented as  $E = 141 \sin(628 t)$ , then the rms value of the voltage and the frequency are respectively
- a) 141 V, 628 Hz                      b) 100 V, 50 Hz                      c) 100 V, 100 Hz                      d) 141 V, 100 Hz
306. Q-factor can be increased by having a coil of
- a) Large inductance, small ohmic resistance  
b) Large inductance, large ohmic resistance  
c) Small inductance, large ohmic resistance  
d) Small inductance, small ohmic resistance
307. A circuit has a resistance of  $12\ \Omega$  and an impedance of  $15\ \Omega$ . The power factor of the circuit will be
- a) 0.8                      b) 0.4                      c) 1.25                      d) 0.125
308. What will be the phase difference between virtual voltage and virtual current, when the current in the circuit is wattless
- a)  $90^\circ$                       b)  $45^\circ$                       c)  $180^\circ$                       d)  $60^\circ$
309. The following series  $L - C - R$  circuit, when driven by an *e.m.f.* source of angular frequency 70 kilo-radians per second, the circuit effectively behaves like



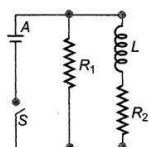- a) Purely resistive circuit                      b) Series  $R - L$  circuit  
c) Series  $R - C$  circuit                      d) Series  $L - C$  circuit with  $R = 0$
310. In AC circuit in which inductance and capacitance are joined in series. Current is found to be maximum when the value of inductance is 0.5 H and the value of capacitance is  $8\ \mu\text{F}$ . The angular frequency of applied alternating voltage will be
- a) 4000 Hz                      b) 5000 Hz                      c)  $2 \times 10^5\text{ Hz}$                       d) 500 Hz
311. Average power generated in an inductor connected to an AC source is
- a)  $\frac{1}{2} Li^2$                       b)  $Li^2$                       c) Zero                      d) None of these
312. In general in an alternating current circuit
- a) The average value of current is zero  
b) The average value of square of the current is zero  
c) Average power dissipation is zero  
d) The phase difference between voltage and current is zero
313. An inductor of inductance  $L = 400\text{ mH}$  and resistors of resistances  $R_1 = 4\ \Omega$  and  $R_2 = 2\ \Omega$  are connected to battery of emf 12 V as shown in the figure. The internal resistance of the battery is negligible. The switch  $S$  is closed at  $t = 0$ . The potential drop across  $L$  as a function of time is



- a)  $6e^{-5t}\text{ V}$                       b)  $\frac{12}{t} e^{-3t}\text{ V}$                       c)  $6(1 - e^{-t/0.2})\text{ V}$                       d)  $12 e^{-5t}\text{ V}$

314. In an AC circuit, the current lags behind the voltage by  $\pi/3$ . The components of the circuit are

- a)  $R$  and  $L$                       b)  $L$  and  $C$                       c)  $R$  and  $C$                       d) Only  $R$

315. The natural frequency ( $\omega_0$ ) of oscillations in  $L - C$  circuit is given by

- a)  $\frac{1}{2\pi\sqrt{LC}}$                       b)  $\frac{1}{2\pi}\sqrt{LC}$                       c)  $\frac{1}{\sqrt{LC}}$                       d)  $\sqrt{LC}$


316. The inductive reactance of an inductor of  $\frac{1}{\pi}$  henry at 50 Hz frequency is

- a)  $\frac{50}{\pi}$  ohm                      b)  $\frac{\pi}{50}$  ohm                      c) 100 ohm                      d) 50 ohm

317. An alternating voltage is represented as  $E = 20 \sin 300t$ . The average value of voltage over one cycle will be

- a) Zero                      b) 10 volt                      c)  $20\sqrt{2}$  volt                      d)  $\frac{20}{\sqrt{2}}$  volt

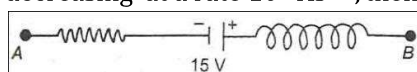318. The network shown in figure is part of a complete circuit. If at a certain instant, the current  $i$  is 5 A and is decreasing at a rate  $10^3 \text{ As}^{-1}$ , then  $(V_B - V_A)$  is



- a) 20 V                      b) 15 V                      c) 10 V                      d) 5 V






319. The coil of choke in a circuit

- a) Increases the current                      b) Decreases the current  
c) Do not change the current                      d) Has high resistance to dc circuit

320. When current in a coil changes from 2 A to 4 A in 0.05s, an emf of 8 V is induced in the coil. Self inductance of the coil is

- a) 0.1 H                      b) 0.2 H                      c) 0.4 H                      d) 0.8 H

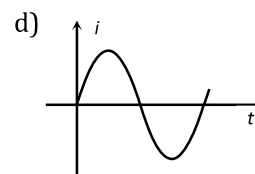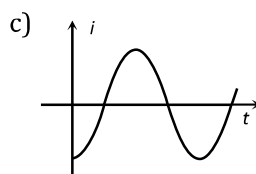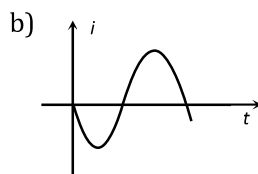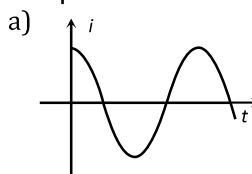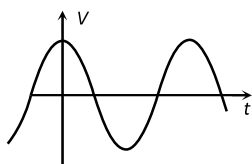321. The voltage across a pure inductor is represented by the following diagram. Which of the following diagrams will represent the current



322. A solenoid has 2000 turns wound over a length of 0.30 m. The area of its cross section is  $1.2 \times 10^{-3} \text{ m}^2$ . Around its central section, a coil of 300 turns is wound. If an initial current of 2 A in the solenoid is reversed in 0.25 s, then the emf induced in the coil is equal to

- a)  $6 \times 10^{-4} \text{ V}$                       b)  $4.8 \times 10^{-2} \text{ V}$                       c)  $6 \times 10^{-2} \text{ V}$                       d) 48 kV

323. In an  $LCR$  series resonant circuit which one of the following cannot be the expression for the Q-factor

- a)  $\frac{\omega L}{R}$                       b)  $\frac{1}{\omega CR}$                       c)  $\sqrt{\frac{L}{C}} \frac{1}{R}$                       d)  $\frac{R}{LC}$

324. A coil has resistance 30 ohm and inductive reactance 20 Ohm at 50 Hz frequency. If ac source, of 200 volt, 100 Hz, is connected across the coil, the current in the coil will be


- a)  $\frac{20}{\sqrt{13}} \text{ A}$                       b) 2.0A                      c) 4.0A                      d) 8.0A

325. The current which does not contribute to the power consumed in an AC circuit is called


- a) non-ideal current                      b) wattles current  
c) convectional current                      d) inductance current

326. An ac circuit consists of an inductor of inductance  $0.5\text{ H}$  and a capacitor of capacitance  $8\text{ }\mu\text{F}$  in series. The current in the circuit is maximum when the angular frequency of ac source is  
 a)  $500\text{ rad/sec}$                       b)  $2 \times 10^5\text{ rad/sec}$                       c)  $4000\text{ rad/sec}$                       d)  $5000\text{ rad/sec}$
327. In a choke coil, the reactance  $X_L$  and resistance  $R$  are such that  
 a)  $X_L = R$                       b)  $X_L \gg R$                       c)  $X_L \ll R$                       d)  $X_L = \infty$
328. In a purely resistive ac circuit, the current  
 a) Lags behind the *e.m.f.* in phase  
 b) Is in phase with the *e.m.f.*  
 c) Leads the *e.m.f.* in phase  
 d) Leads the *e.m.f.* in half the cycle and lags behind it in the other half
329. The coefficient of induction of a choke coil is  $0.1\text{ H}$  and resistance is  $12\Omega$ . If it is connected to an alternating current source of frequency  $60\text{ Hz}$ , then power factor will be  
 a) 0.32                      b) 0.30                      c) 0.28                      d) 0.24
330. Two coil  $X$  and  $Y$  are placed in a circuit such that a current changes by  $2\text{ A}$  in coil  $X$  and magnetic flux change of  $0.4\text{ Wb}$  occurs in  $Y$ . The value of mutual inductance of the coils is  
 a)  $0.8\text{ H}$                       b)  $0.2\text{ Wb}$                       c)  $0.2\text{ H}$                       d)  $5\text{ H}$
331. A lamp consumes only 50% of peak power in an a.c. circuit. What is the phase difference between the applied voltage and the circuit current  
 a)  $\frac{\pi}{6}$                       b)  $\frac{\pi}{3}$                       c)  $\frac{\pi}{4}$                       d)  $\frac{\pi}{2}$
332. Reactance of a capacitor of capacitance  $C\text{ }\mu\text{F}$  for ac frequency  $\frac{400}{\pi}\text{ Hz}$  is  $25\Omega$ . The value  $C$  is  
 a)  $50\text{ }\mu\text{F}$                       b)  $25\text{ }\mu\text{F}$                       c)  $100\text{ }\mu\text{F}$                       d)  $75\text{ }\mu\text{F}$
333. In a circuit containing an inductance of zero resistance, the *e.m.f.* of the applied ac voltage leads the current by  
 a)  $90^\circ$                       b)  $45^\circ$                       c)  $30^\circ$                       d)  $0^\circ$
334. When a DC voltage of  $200\text{ V}$  is applied to a coil of self-inductance  $\left(\frac{2\sqrt{3}}{\pi}\right)\text{ H}$ , a current of  $1\text{ A}$  flows through it. But by replacing DC source with AC source of  $200\text{ V}$ , the current in the coil is reduced to  $0.5\text{ A}$ . Then the frequency of AC supply is  
 a)  $100\text{ Hz}$                       b)  $75\text{ Hz}$                       c)  $60\text{ Hz}$                       d)  $50\text{ Hz}$
335. Voltage and current in an ac circuit are given by  
 $V = 5 \sin\left(100\pi t - \frac{\pi}{6}\right)$  and  $I = 4 \sin\left(100\pi t + \frac{\pi}{6}\right)$   
 a) Voltage leads the current by  $30^\circ$                       b) Current leads the voltage by  $30^\circ$   
 c) Current leads the voltage by  $60^\circ$                       d) Voltage leads the current by  $60^\circ$
336. A virtual current of  $4\text{ A}$  and  $50\text{ Hz}$  flows in an ac circuit containing a coil. The power consumed in the coil is  $240\text{ W}$ . If the virtual voltage across the coil is  $100\text{ V}$  its inductance will be  
 a)  $\frac{1}{3\pi}\text{ H}$                       b)  $\frac{1}{5\pi}\text{ H}$                       c)  $\frac{1}{7\pi}\text{ H}$                       d)  $\frac{1}{9\pi}\text{ H}$
337. An ac generator, produces an output voltage  $E = 170 \sin 377 t$  volts, where  $t$  is in seconds. The frequency of ac voltage is  
 a)  $50\text{ Hz}$                       b)  $110\text{ Hz}$                       c)  $60\text{ Hz}$                       d)  $230\text{ Hz}$
338. An alternating voltage is connected in series with a resistance  $R$  and an inductance  $L$ . If the potential drop across the resistance is  $200\text{ V}$  and across the inductance is  $150\text{ V}$ , then the applied voltage is  
 a)  $350\text{ V}$                       b)  $250\text{ V}$                       c)  $500\text{ V}$                       d)  $300\text{ V}$
339. An  $LCR$  series ac circuit is at resonance with  $10\text{ V}$  each across  $L$ ,  $C$  and  $R$ . If the resistance is halved, the respective voltage across  $L$ ,  $C$  and  $R$  are  
 a)  $10\text{ V}$ ,  $10\text{ V}$  and  $5\text{ V}$                       b)  $10\text{ V}$ ,  $10\text{ V}$  and  $10\text{ V}$                       c)  $20\text{ V}$ ,  $20\text{ V}$  and  $5\text{ V}$                       d)  $20\text{ V}$ ,  $20\text{ V}$  and  $10\text{ V}$
340. The peak value of an alternating current is  $5\text{ A}$  and its frequency is  $60\text{ Hz}$ . Find its rms value and time taken to reach the peak value of current starting from zero.

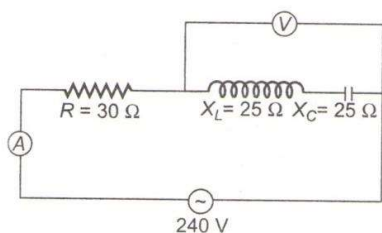- a) 3.536A; 4.167 ms      b) 3.536 A; 15 ms      c) 6.07 A; 10 ms      d) 2.536 A; 4.167 ms
341. If a current of 3 A flowing in the primary coil is reduced to zero in 0.001 s, the induced emf in between the two coils is 15000 V, the coefficient of mutual induction is  
a) 0.5 H      b) 5 H      c) 1.5 H      d) 10 H
342. If  $L$  and  $R$  represent inductance and resistance respectively, then dimension of  $L/R$  will be  
a)  $[ML^0T^0]$       b)  $[M^0L^0T^{-1}]$       c)  $[M^0L^0T^{-2}]$       d)  $[M^0LT^{-2}]$
343. A low-loss transformer has 230 V applied to the primary and gives 4.6 V in the secondary. Secondary is connected to a load, which draws 5 A of current. The current (in ampere) in the primary is  
a) 0.1      b) 1.0      c) 10      d) 250
344. In the circuit shown in figure neglecting source resistance, the voltmeter and ammeter readings will be respectively



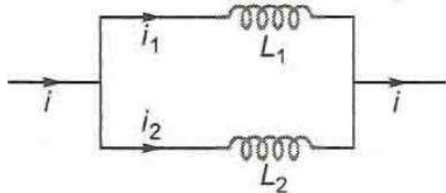- a) 0 V, 3 A      b) 150 V, 3 A      c) 150 V, 6 A      d) 0 V, 8 A
345. The current  $i$  in the circuit shown here varies with time  $t$  is
- 
- a)      b)      c)      d)
346. A 20 volts ac is applied to a circuit consisting of a resistance and a coil with negligible resistance. If the voltage across the resistance is 12 V, the voltage across the coil is  
a) 16 volts      b) 10 volts      c) 8 volts      d) 6 volts
347. The resistance of a coil for dc is in ohms. In ac, the resistance  
a) Will remain same      b) Will increase      c) Will decrease      d) Will be zero
348. The natural frequency of an  $L - C$  circuit is 125000 cycle/s. Then the capacitor  $C$  is replaced by another capacitor with a dielectric medium of dielectric constant  $K$ . In this case, the frequency decreases by 25 kHz. The value of  $K$  is  
a) 3.0      b) 2.1      c) 1.56      d) 1.7
349. A light bulb is rated 100 W for a 220 V supply. The resistance of the bulb and the peak voltage of the source respectively are  
a) 242 Ω and 311 V      b) 484 Ω and 311 V      c) 484 Ω and 440 V      d) 242 Ω and 440 V
350. Two inductors  $L_1$  and  $L_2$  are connected in parallel and a time varying current flows as shown in figure. The ratio of currents  $i_1/i_2$  at any time  $t$  is




- a)  $L_2/L_1$                       b)  $L_1/L_2$                       c)  $\frac{L_2^2}{(L_1 + L_2)^2}$                       d)  $\frac{L_1^2}{(L_1 + L_2)^2}$

351. An  $LCR$  series circuit is at resonance. Then

- a) The phase difference between current and voltage is  $90^\circ$   
 b) The phase difference between current and voltage is  $45^\circ$   
 c) Its impedance is purely resistive  
 d) Its impedance is zero

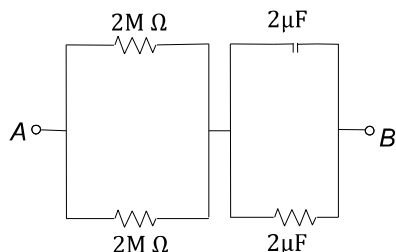352. At time  $t = 0$ , a battery of 10 V is connected across points  $A$  and  $B$  in the given circuit. If the capacitors have no charge initially, at what time (in second) does the voltage across them become 4 V?  
 (Take  $\ln 5 = 1.6$ ,  $\ln 3 = 1.1$ )




- a) 2                      b) 3                      c) 2.5                      d)  $\frac{3}{2}$

353. A coil of  $200\Omega$  resistance and  $0.1 H$  inductance is connected to an ac source of frequency  $200/2\pi Hz$ . Phase angle between potential and current will be

- a)  $30^\circ$                       b)  $90^\circ$                       c)  $45^\circ$                       d)  $0^\circ$

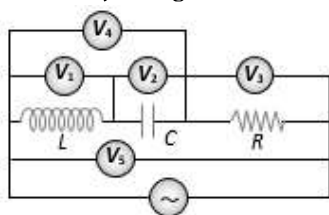354. In the adjoining ac circuit the voltmeter whose reading will be zero at resonance is



- a)  $V_1$                       b)  $V_2$                       c)  $V_3$                       d)  $V_4$

355. In an ac circuit the reactance of a coil is  $\sqrt{3}$  times its resistance, the phase difference between the, voltage across the coil to the current through the coil will be

- a)  $\pi/3$                       b)  $\pi/2$                       c)  $\pi/4$                       d)  $\pi/6$

356. adsf

- a) 122                      b) 3                      c) 4                      d) 5

357. If 25 A current is drawn by 220 V motor and back emf produced is 80 V, the value of armature resistance is

- a)  $56\Omega$                       b)  $5.6\Omega$                       c)  $0.56\Omega$                       d)  $0.5\Omega$

358. In a pure inductive circuit **or** In an ac circuit containing inductance only, the current

- a) Leads the  $e.m.f.$  by  $90^\circ$                       b) Lags behind the  $e.m.f.$  by  $90^\circ$   
 c) Sometimes leads and sometimes lags behind the  $e.m.f.$                       d) Is in phase with the  $e.m.f.$

359. Two conducting circular loops of radii  $R_1$  and  $R_2$  are placed in the same plane with their centres coinciding. If  $R_1 > R_2$ , the mutual inductance  $M$  between them will be directly proportional to

- a)  $\frac{R_1}{R_2}$                       b)  $\frac{R_2}{R_1}$                       c)  $\frac{R_1^2}{R_2}$                       d)  $\frac{R_2^2}{R_1}$

360. Two circuits have mutual inductance of 0.09 H. Average emf induced in the secondary by a change of current from 0 to 20 A in 0.006 s in primary will be

- a) 120 V                      b) 200 V                      c) 180 V                      d) 300 V

361. In an  $LR$ -circuit, the inductive reactance is equal to the resistance  $R$  of the circuit. An  $e.m.f.$   $E = E_0 \cos(\omega t)$




is applied to the circuit. The power consumed in the circuit is

- a)  $\frac{E_0^2}{R}$                       b)  $\frac{E_0^2}{2R}$                       c)  $\frac{E_0^2}{4R}$                       d)  $\frac{E_0^2}{8R}$

362. In  $L - R$  circuit, resistance is  $8 \Omega$  and inductive reactance is  $6 \Omega$ , then impedance is

- a)  $2 \Omega$                       b)  $14 \Omega$                       c)  $4 \Omega$                       d)  $10 \Omega$

363. Is it possible

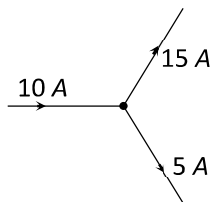


- a) Yes                      b) No  
c) Cannot be predicted                      d) Insufficient data to reply

364. In the transmission of a.c. power through transmission lines, when the voltage is stepped up  $n$  times, the power loss in transmission

- a) Increases  $n$  times                      b) Decreases  $n$  times  
c) Increases  $n^2$  times                      d) Decreases  $n^2$  times

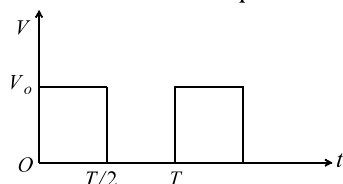365. The r. m. s. value of potential difference  $V$  shown in the figure is



- a)  $V_0/2$                       b)  $V_0/\sqrt{3}$                       c)  $V_0$                       d)  $V_0/\sqrt{2}$


366. Mutual inductance of two coils can be increased by

- a) Decreasing the number of turns in the coils                      b) Increasing the number of turns in the coils  
c) Winding the coils on wooden cores                      d) None of the above

367. In a circuit  $L$ ,  $C$  and  $R$  are connected in series with an alternating voltage source of frequency  $f$ . The current leads the voltage by  $45^\circ$ . The value of  $C$  is

- a)  $\frac{1}{2\pi f (2\pi f L + R)}$                       b)  $\frac{1}{\pi f (2\pi f L + R)}$                       c)  $\frac{1}{2\pi f (2\pi f L - R)}$                       d)  $\frac{1}{\pi f (2\pi f L - R)}$

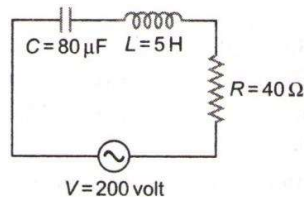368. From figure shown below a series  $L - C - R$  circuit connected to a variable frequency  $200 \text{ V}$  source.  $C = 80 \mu\text{F}$  and  $R = 40 \Omega$ . Then the source frequency which drive the circuit at resonance is



- a)  $25 \text{ Hz}$                       b)  $\frac{25}{\pi} \text{ Hz}$                       c)  $50 \text{ Hz}$                       d)  $\frac{50}{\pi} \text{ Hz}$

369. A coil is wound on a core of rectangular cross-section. If all the linear dimensions of core are increased by a factor 2 and number of turns per unit length of coil remains same, the self-inductance increases by a factor of

- a) 16                      b) 8                      c) 4                      d) 2

370. A choke is preferred to a resistance for limiting current in AC circuit because

- a) Choke is cheap                      b) There is no wastage of power  
c) Choke is compact in size                      d) Choke is a good absorber of heat

371. An AC voltage source of variable angular frequency  $\omega$  and fixed amplitude  $V_0$  is connected in series with a



capacitance  $C$  and an electric bulb of resistance  $R$  (inductance zero). When  $\omega$  is increased

- |  |   |
|--|---|
| a) The bulb glows dimmer                       | b) The bulb glows brighter                  |
| c) Total impedance of the circuit is unchanged | d) Total impedance of the circuit increases |

